

# Microrredes Eléctricas

---

# Microrredes Eléctricas



---

Facultad de Ingeniería

---

# 2

# AC Microgrids


1. Introduction.
2. Topological operation of Power Electronics Converters.
  1. Power Inverter.
  2. Syncronization.
  3. Control and operation Topologies.
  4. Interaction of Power Converters



# 1. Introduction

---

## Microgrid

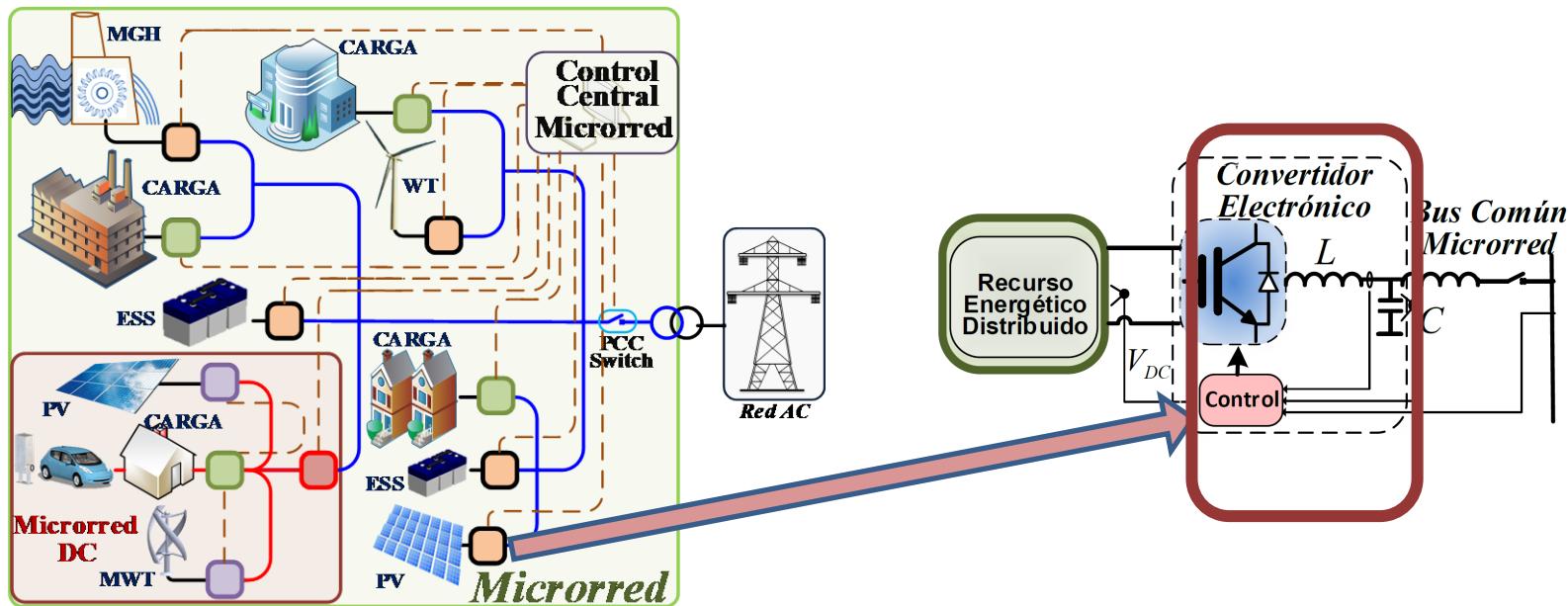

# 1. Introduction

---

## Control Structure for a Microgrid

A control system in a microgrid includes the control functions that define the microgrid as a self-manageable system, capable of operating autonomously or while connected to the grid, as well as the ability to connect and disconnect from the main grid for energy exchange or provision of auxiliary services. It is the sole point of interface with any device within the distributed energy resources (DER) or their management system (DERMS), or the energy management system (EMS). It must have real-time control and energy management functions that operate in the following situations:

- Operate in island mode or connected to the grid.
- Automatic transition from isolated mode to grid-connected mode.
- Resynchronization and reconnection from island mode to grid-connected mode.
- Energy Management System (EMS) for the optimization of active and reactive energy consumption.
- Provide auxiliary functions, grid support, participation in the energy market, and operation of the electrical system.

---

IEEE Standard 20307\_2017

Facultad de Ingeniería




## 1. Introduction

---

# Hierarchical Control Structure in a Microgrid

For the purposes of interconnection, a microgrid will appear to the connected grid as a single controllable entity. The control system is the system that achieves this objective. It meets the interconnection requirements using high-level, central-level, or low-level functions within its operations.


IEEE Standard 20307\_2017

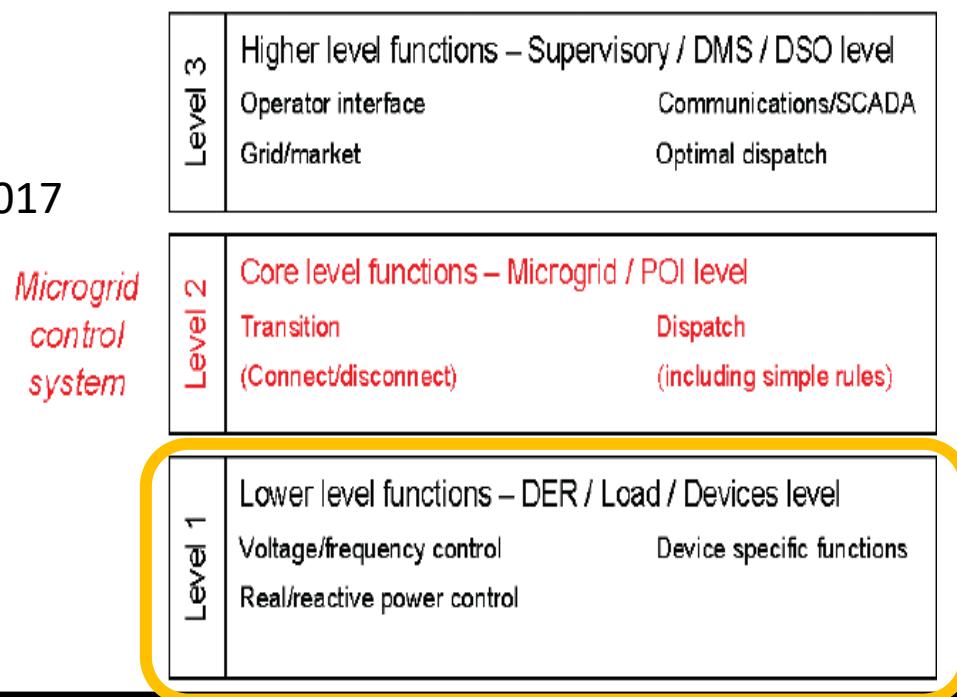

## 1. Introduction

---
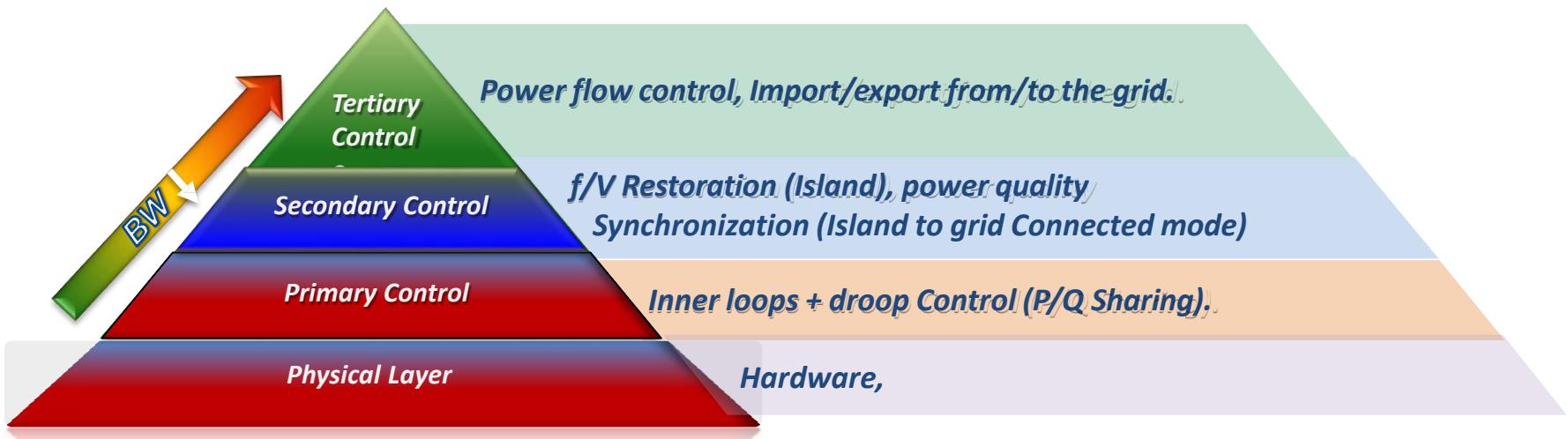
# Hierarchical Control Structure in a Microgrid



J. C. Vasquez, J. M. Guerrero, J. Miret, M. Castilla and L. Garcia de Vicuna, "Hierarchical Control of Intelligent Microgrids," in *IEEE Industrial Electronics Magazine*, vol. 4, no. 4, pp. 23-29, Dec. 2010.



## 2. Power Inverter.

---

# Physical Layer



## 2. Power Inverter.

---

Three phase line.




## 2. Power Inverter.

---

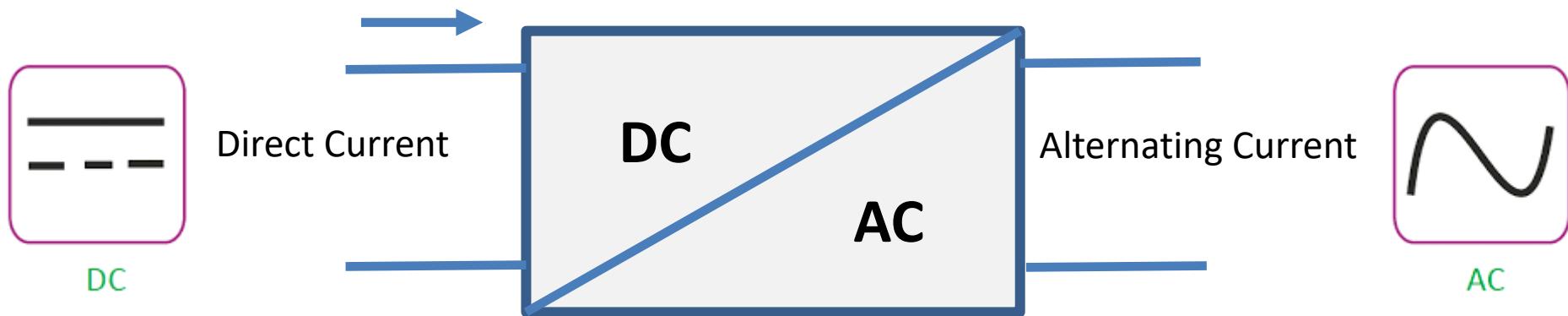
# Inverter.

An inverter is considered any circuit able to transform direct current (DC) into Alternating current (AC).



## 2. Power Inverter.

# Inverter.

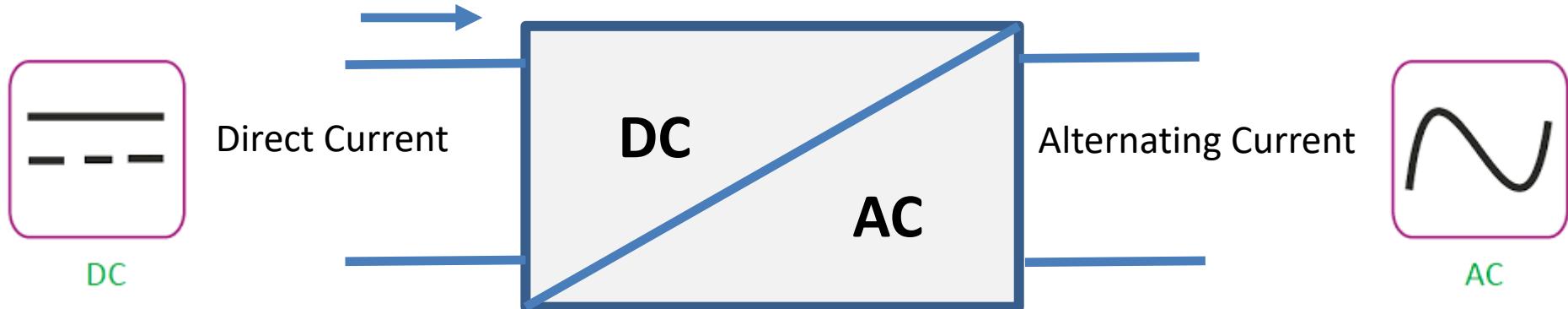

- *IEEE 1547 Interconnection of Distributed Generation.*
- DC/AC Conversion.
- Grid Current Control.
- Grid Synchronization.
- DC Voltage Control.
- Maximum Power Point Tracking (MPPT).
- Islanding Detection.
- Ancillary Support.




## 2. Power Inverter.

---

# Examples.

Wind turbine control structure:

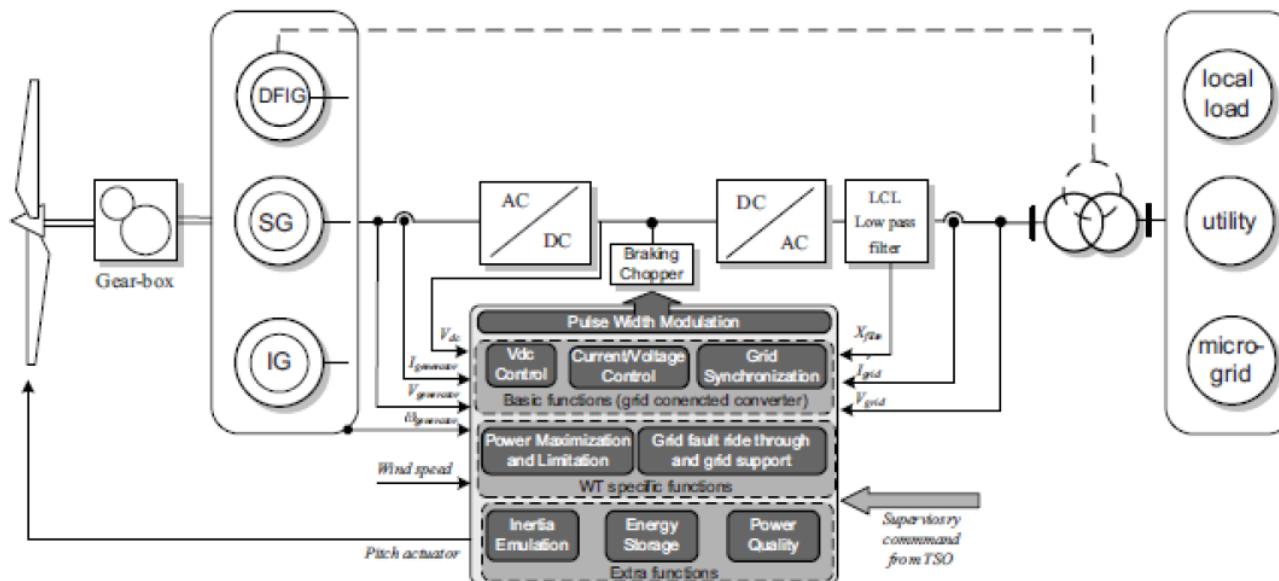


Teodorescu, R., Liserre, M., & Rodriguez, P. (2011). *Grid converters for photovoltaic and wind power systems*. John Wiley & Sons.



## 2. Power Inverter.

---

# Examples.


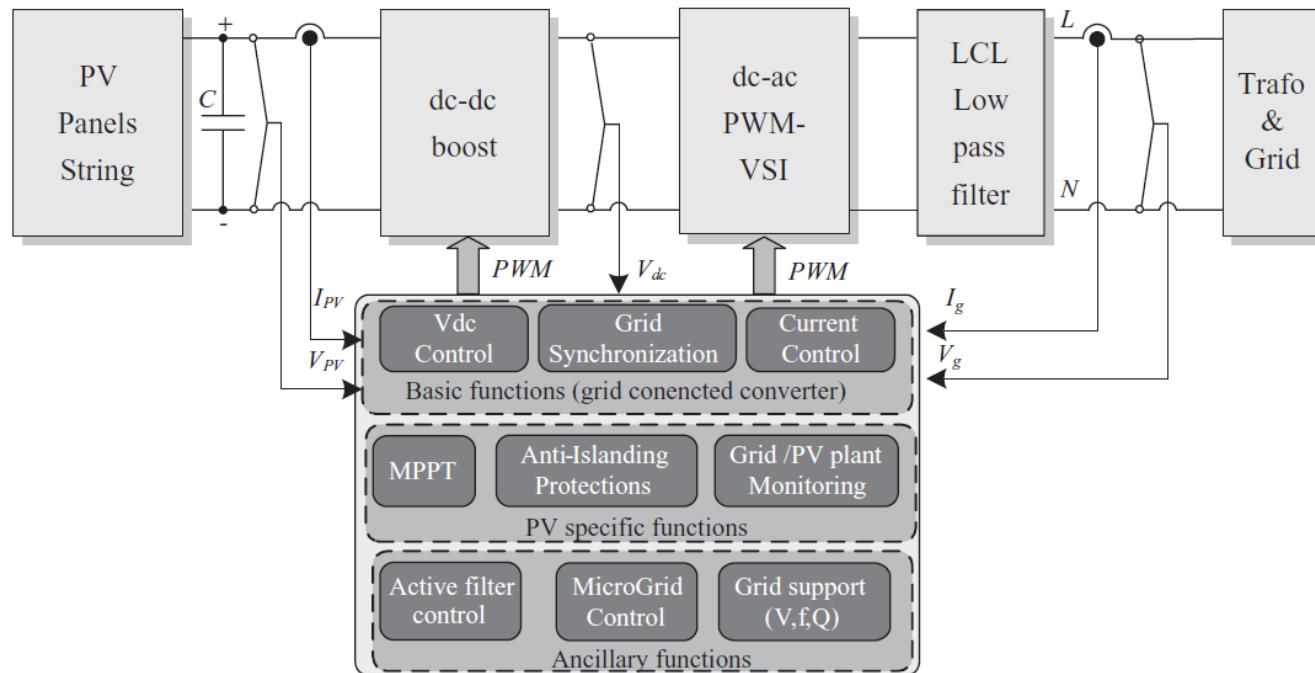


Teodorescu, R., Liserre, M., & Rodriguez, P. (2011). *Grid converters for photovoltaic and wind power systems*. John Wiley & Sons.



## 2. Power Inverter.

# Examples.

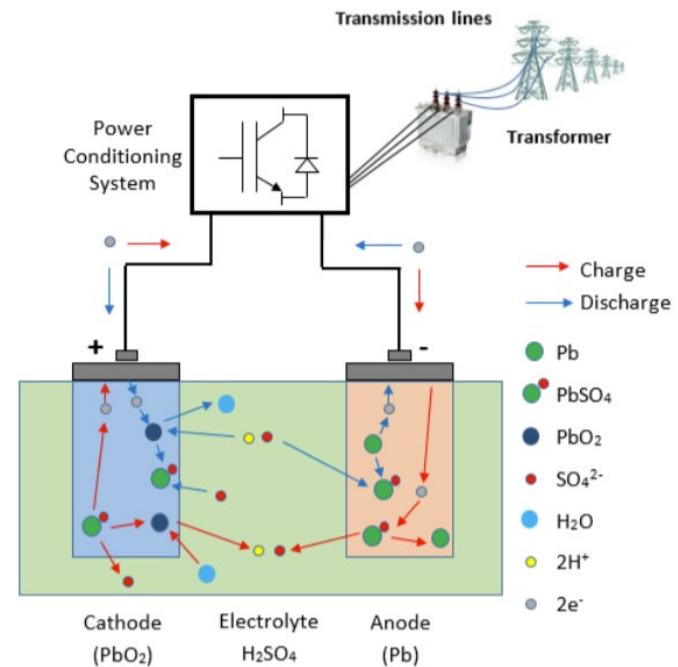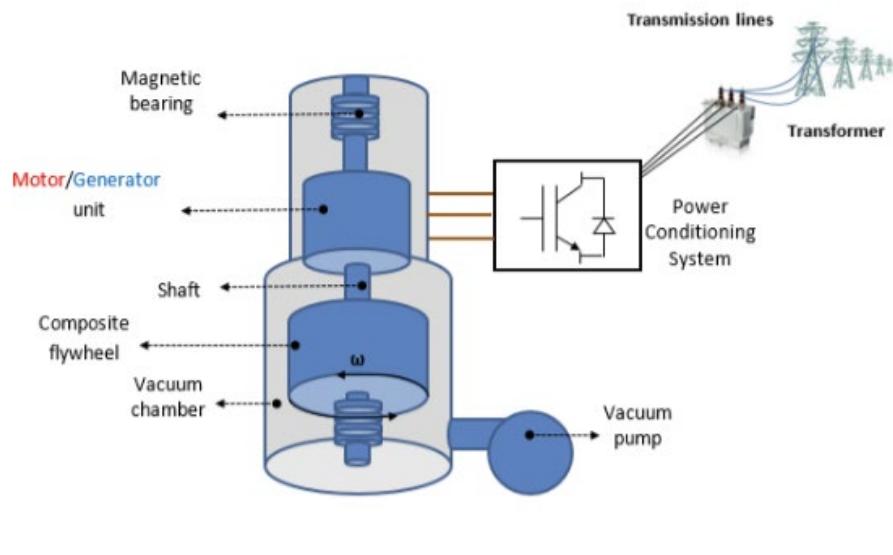


Nikolaidis, Pavlos & Poullikkas, Andreas. (2017). Journal of Power Technologies 97 (3) (2017) 220-245 A comparative review of electrical energy storage systems for better sustainability.



## 2. Power Inverter.

# Examples.

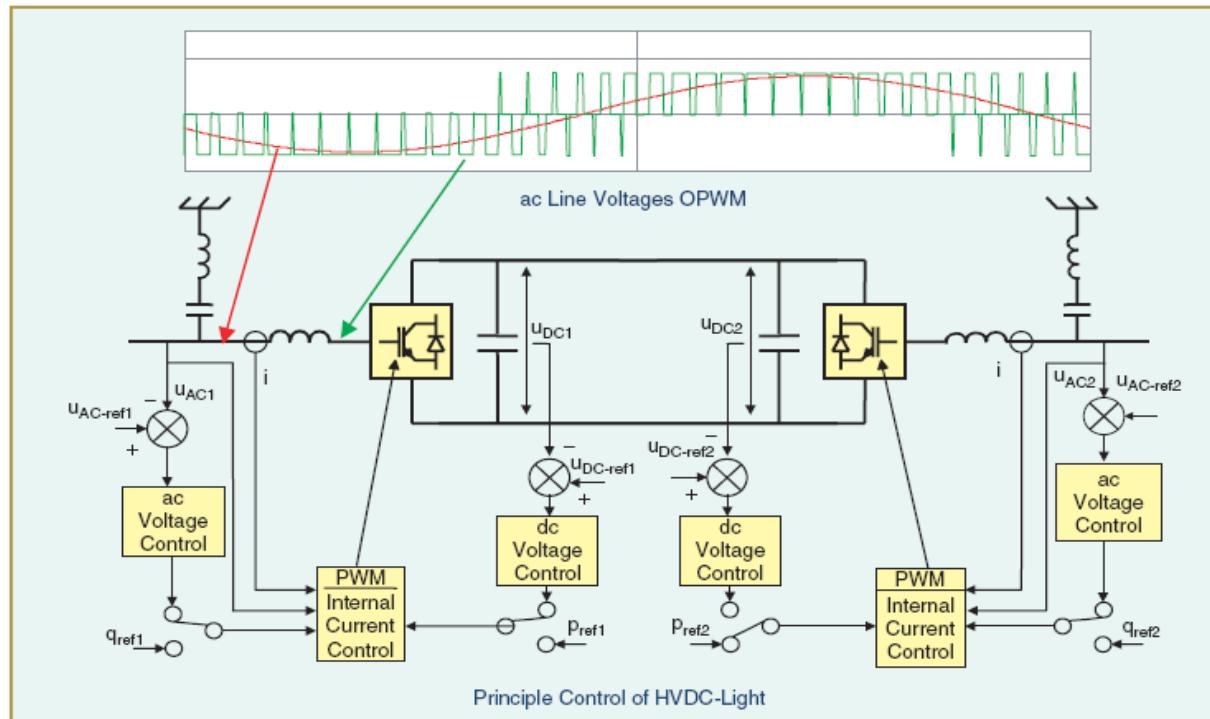




*"The ABC of the HVDC technology"* IEEE Power & Energy Magazine March/April 2007 Vol. 5 No. 2



## 2. Power Inverter.
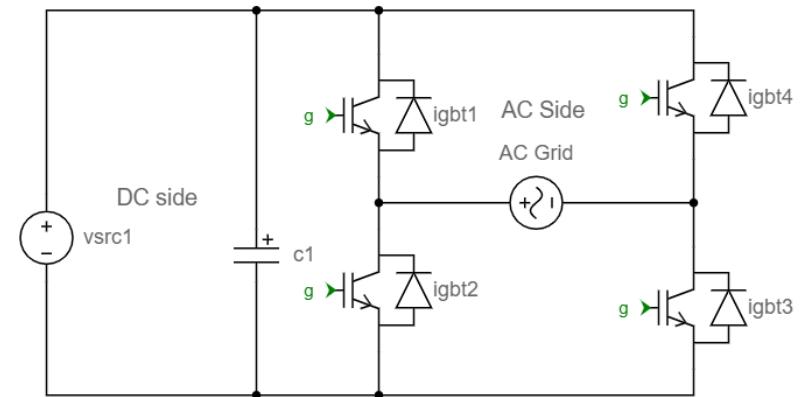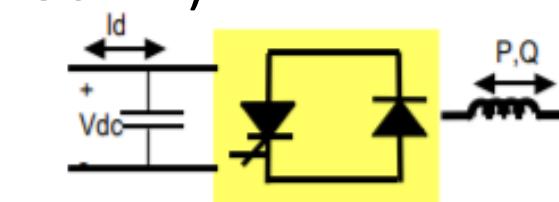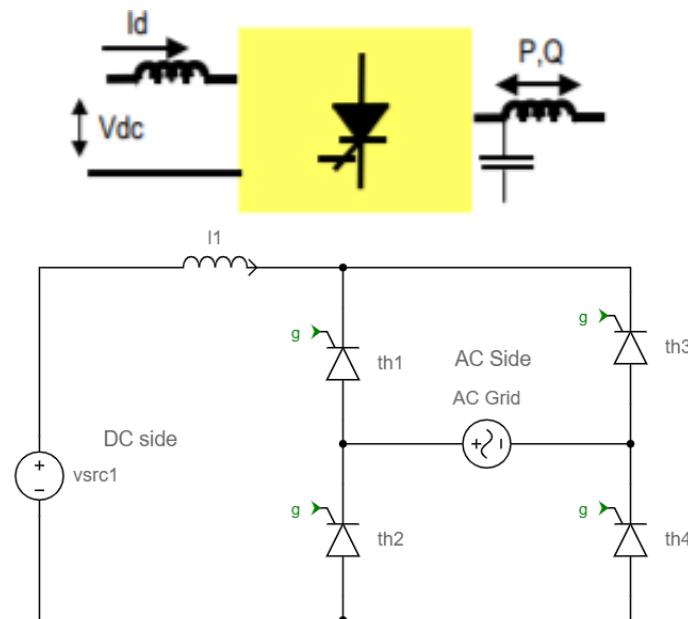
# Power Inverter.

- Current Source Inverter (CSI).
  - Supplied by a constant current.
  - Line commutated switches (Thyristors).
- Voltage Source Inverter (VSI).
  - Supplied by a constant voltage source.
  - Self-commutated switches (IGBT, MOSFET).




## 2. Power Inverter.

---



# Thyristor Based Inverter

- SCR.

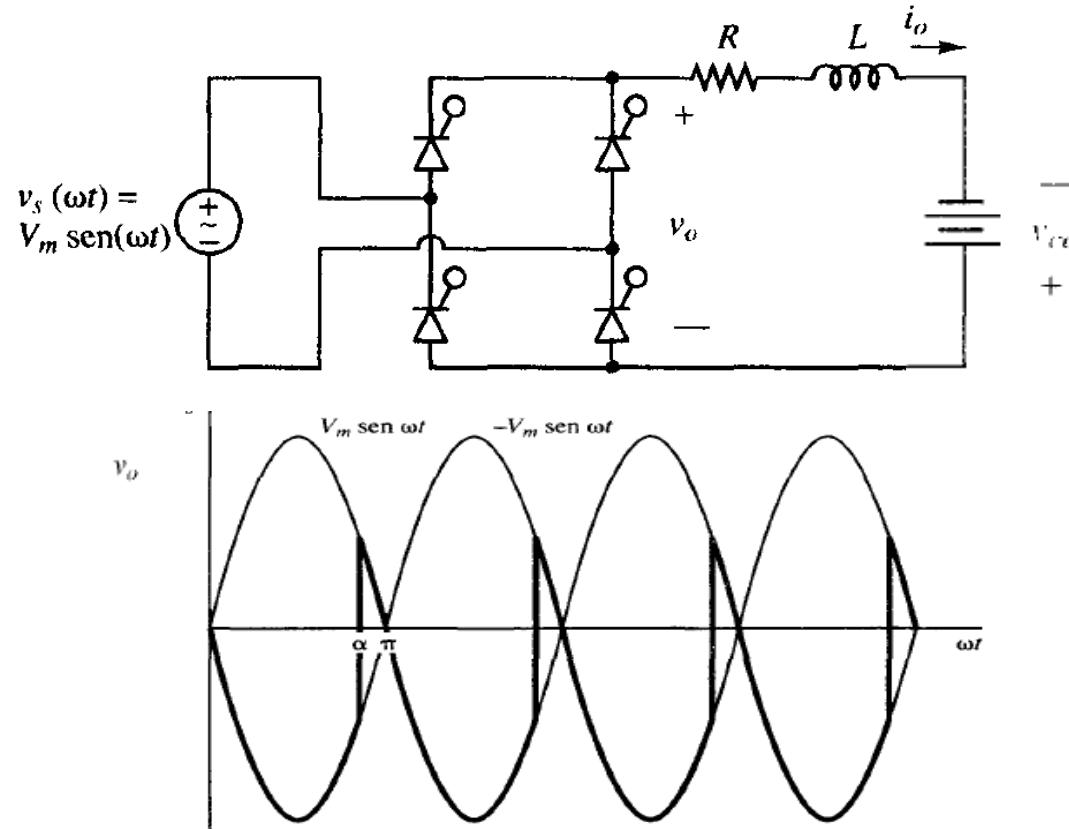

## 2. Power Inverter.

# Thyristor Based Inverter

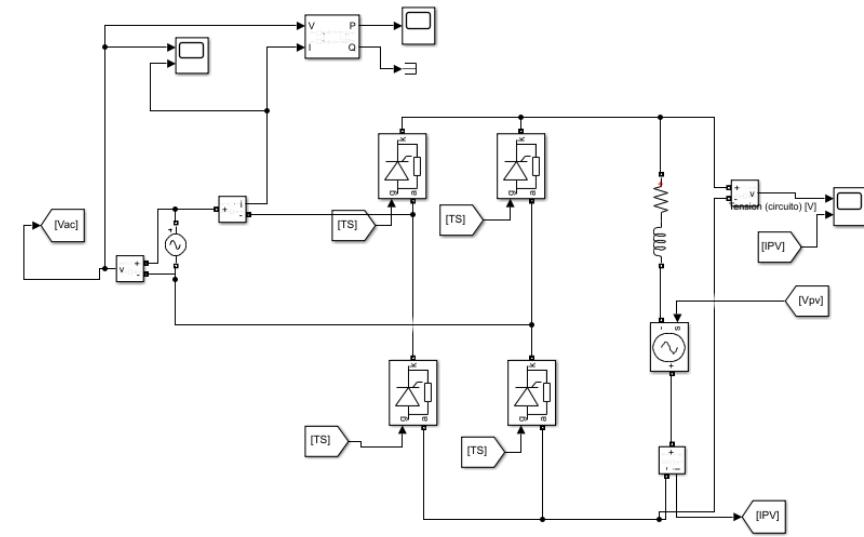
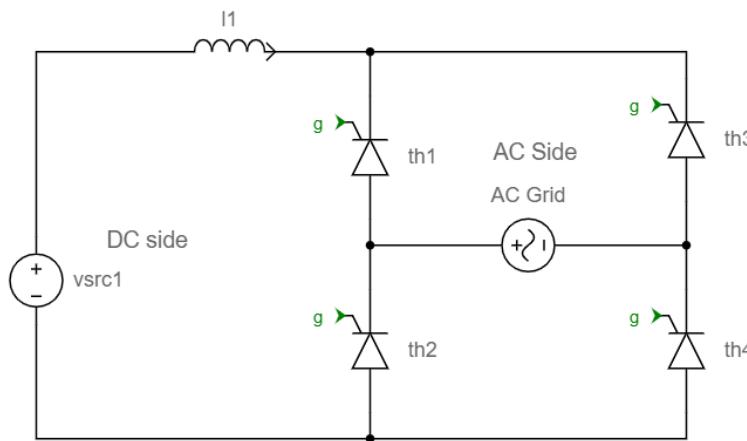


Simulation1 File.



## 2. Power Inverter.



# Self-Commutated Switches

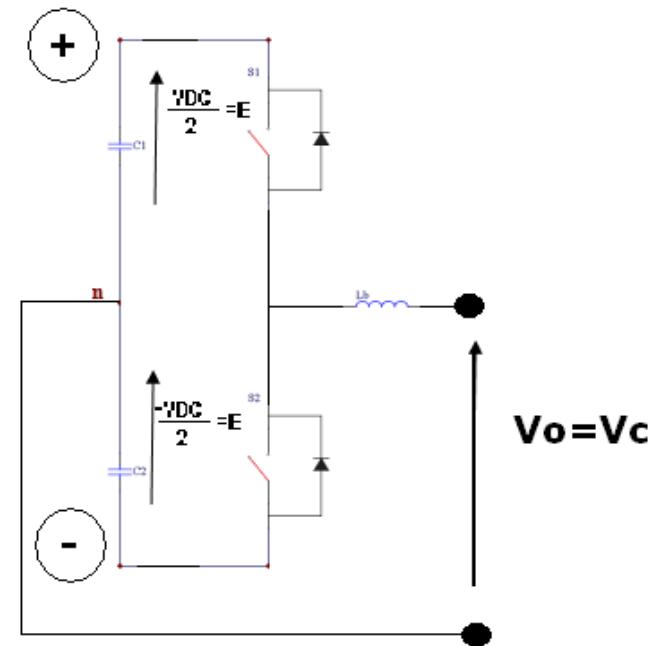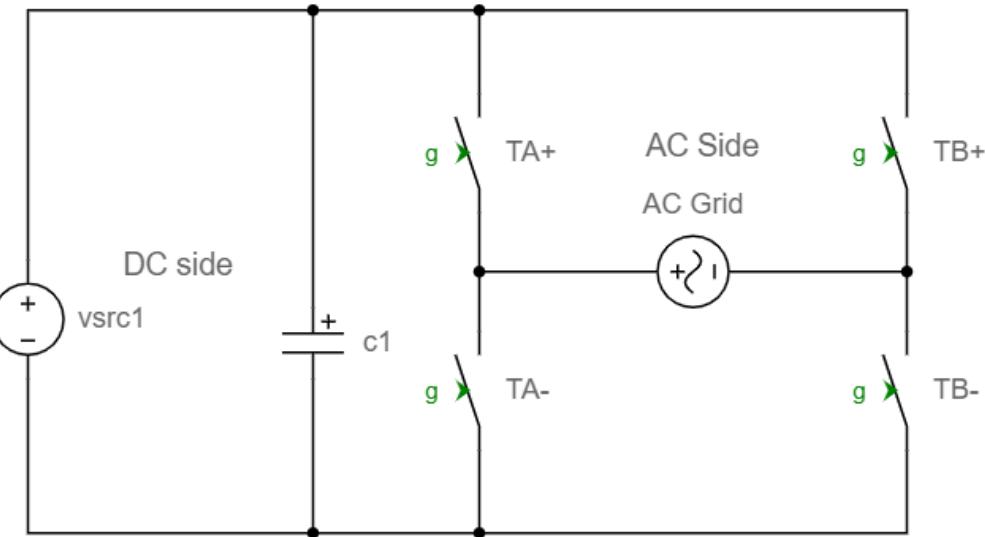

## 2. Power Inverter.



---

PWM

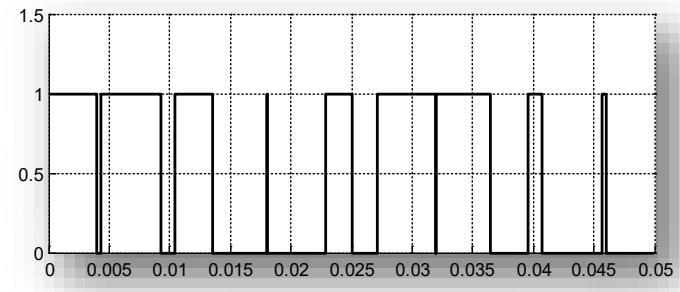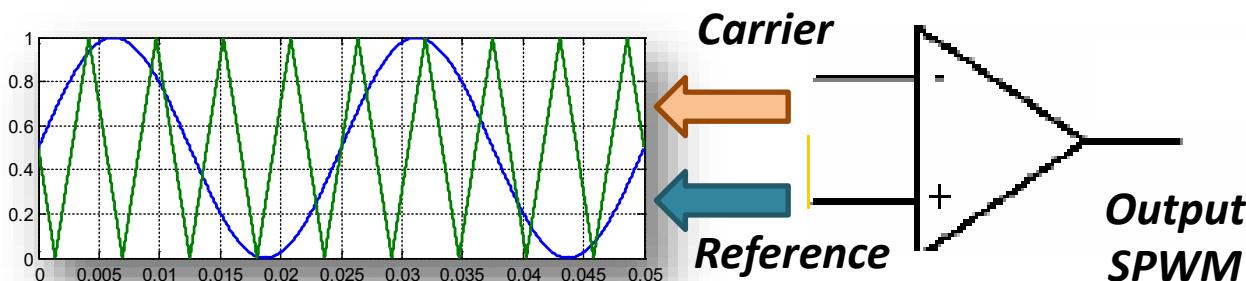






## 2. Power Inverter.

# PWM Modulation

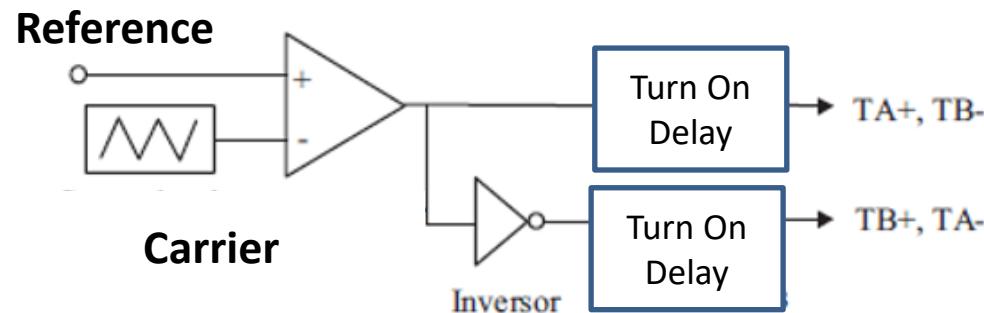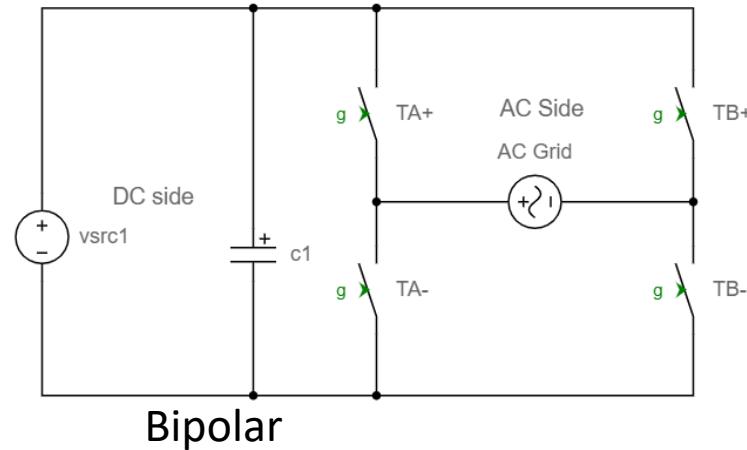


## 2. Power Inverter.

# PWM Modulation

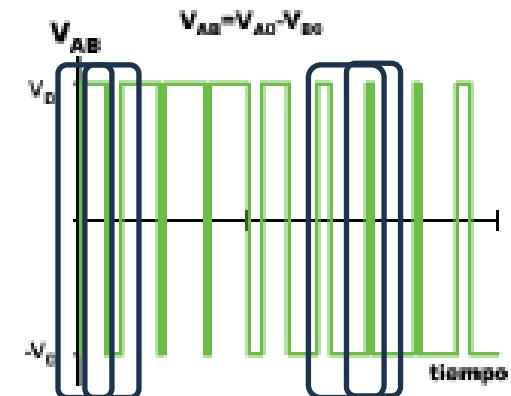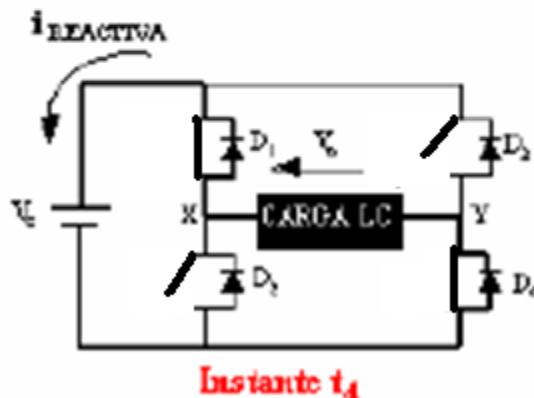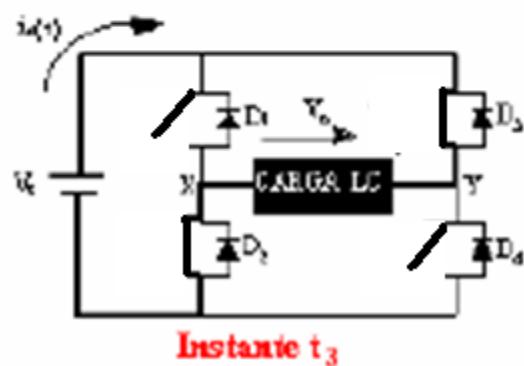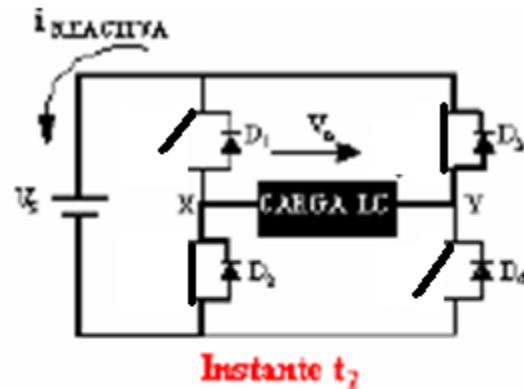
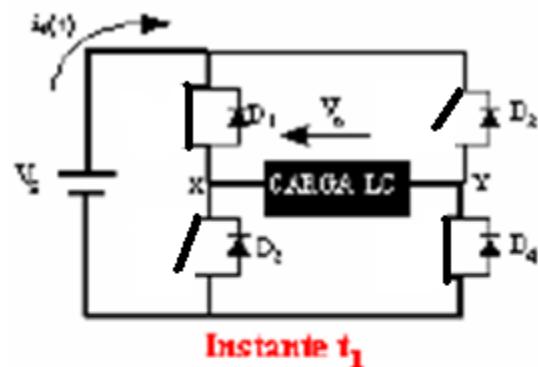


## 2. Power Inverter.

# PWM Modulation

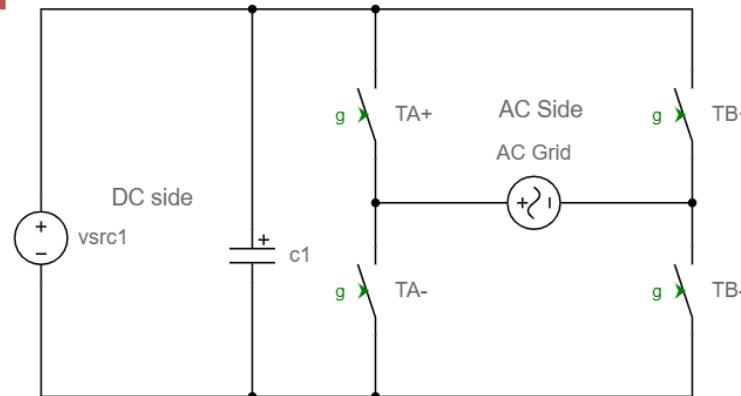


Unipolar



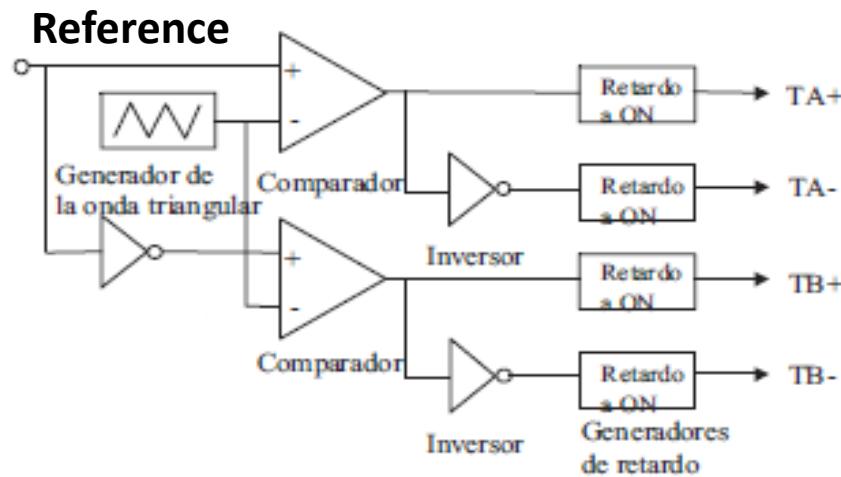
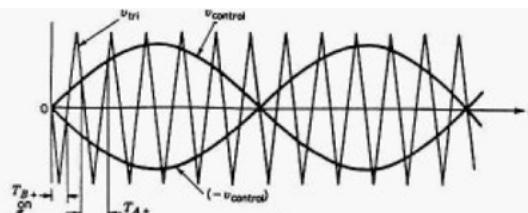


## 2. Power Inverter.





# PWM Modulation

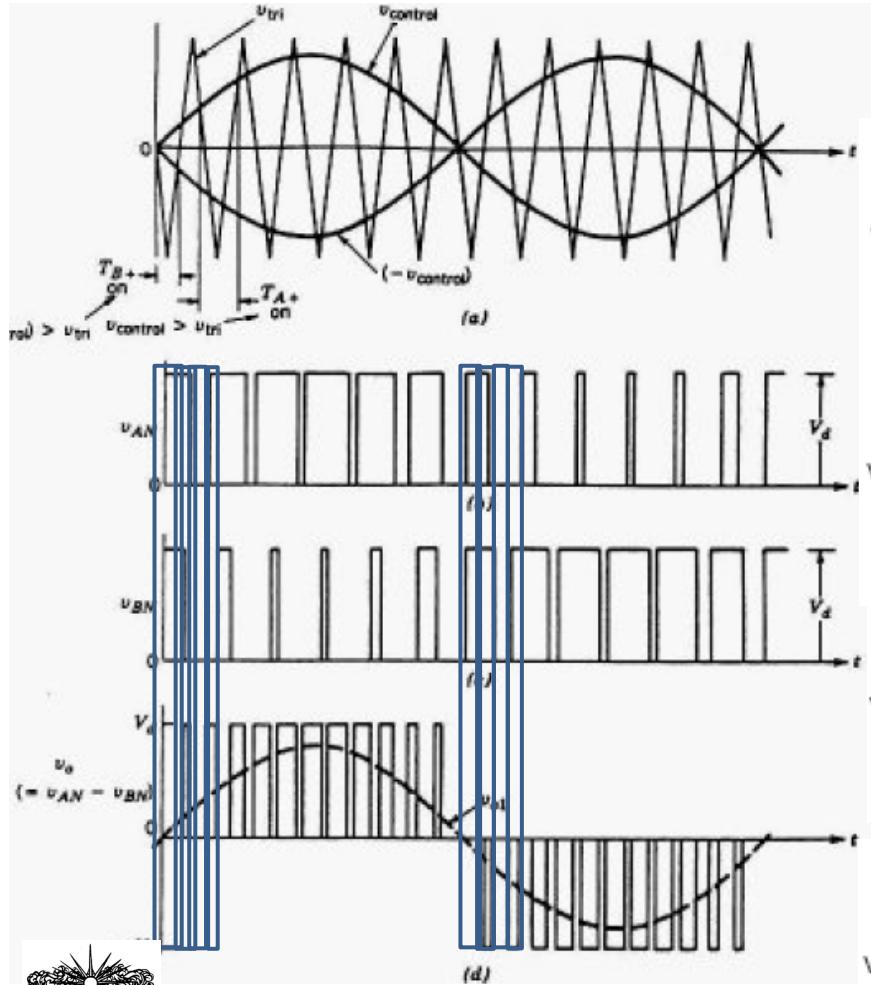

- Positive semi Cycle

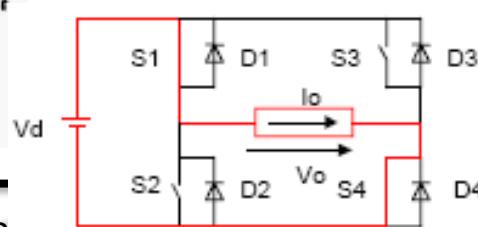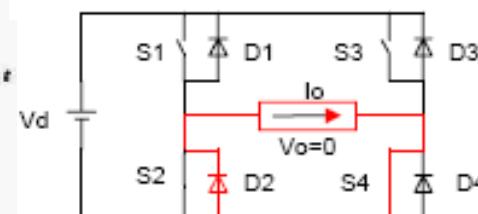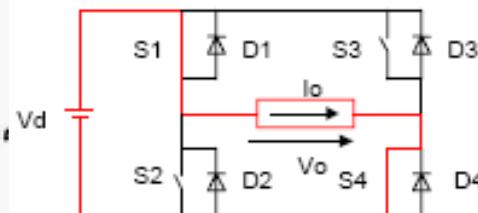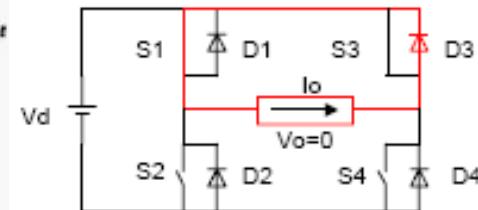


- Negative Semi Cycle

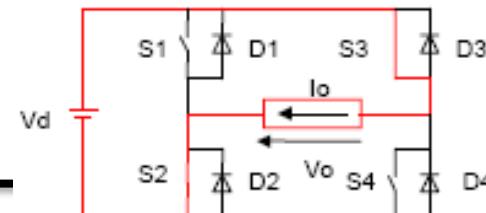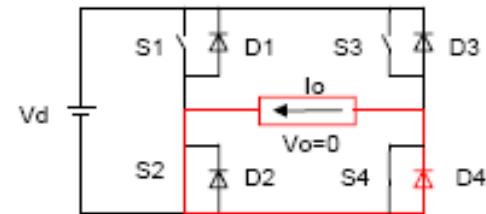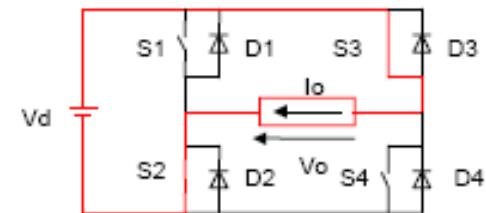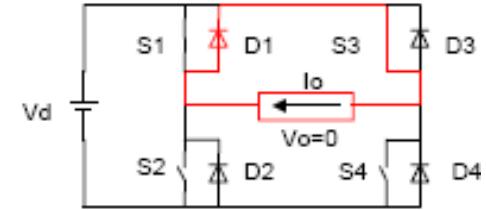

## 2. Power Inverter.

# PWM Modulation

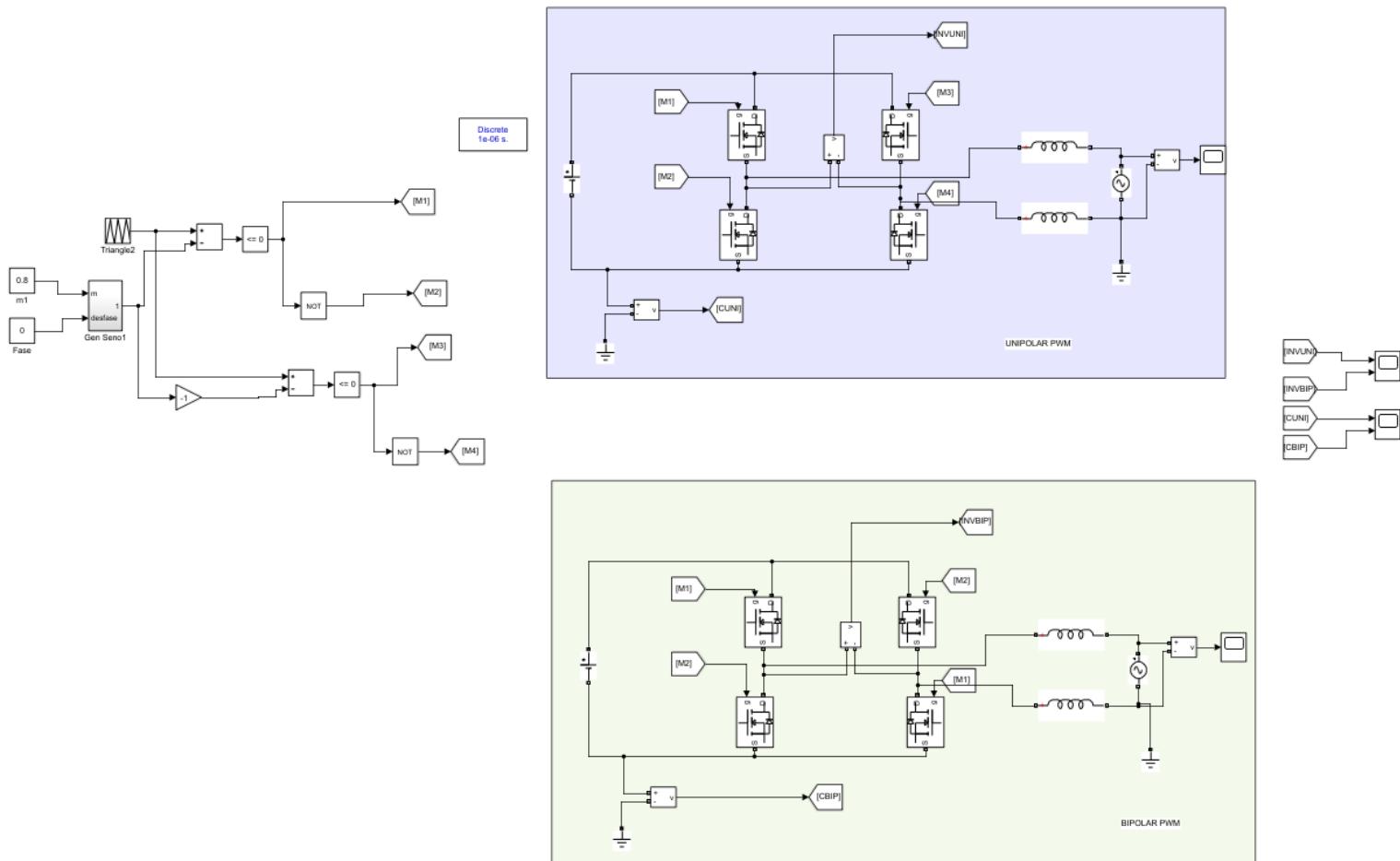

Simulation2 File.

Facultad de Ingeniería




## 2. Power Inverter.

# PWM Modulation

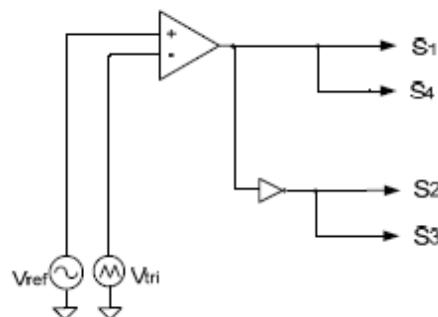
### Bipolar PWM

S1 + S4 and S2 + S3 are switched complementary at high frequency



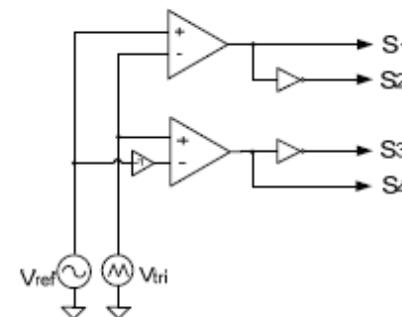
### Unipolar PWM

Leg A and B are switched with high frequency with mirrored sinusoidal ref.



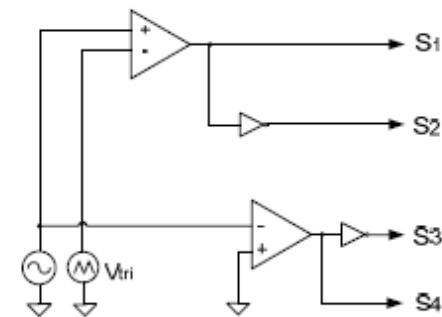
### Hybrid PWM

Leg A is switched with high frequency and Leg B is switched with grid frequency




### Bipolar PWM

Reference and Carrier Signals

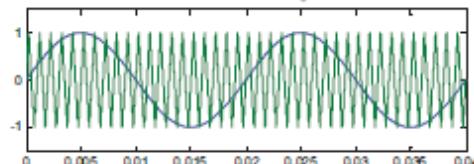


Output voltage

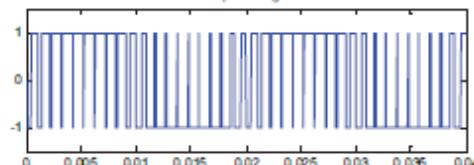


### Unipolar PWM

Reference and Carrier Signals

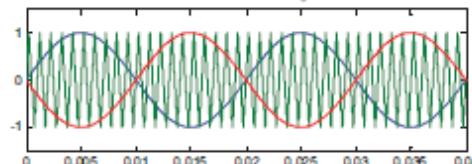


Output voltage

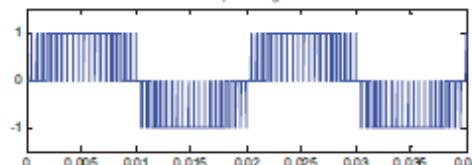


### Hybrid PWM

Reference and Carrier Signals

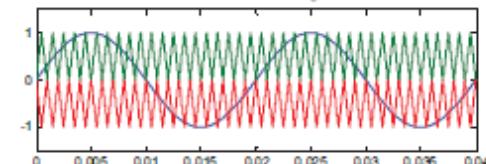

Output voltage



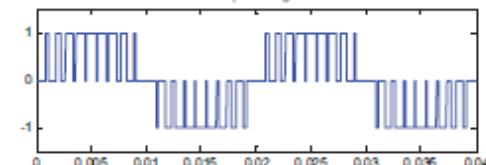


Power Electronics for Renewable Energy Systems Course, Aalborg University

Facultad de Ingeniería

## 2. Power Inverter.



# Three Phase Inverter

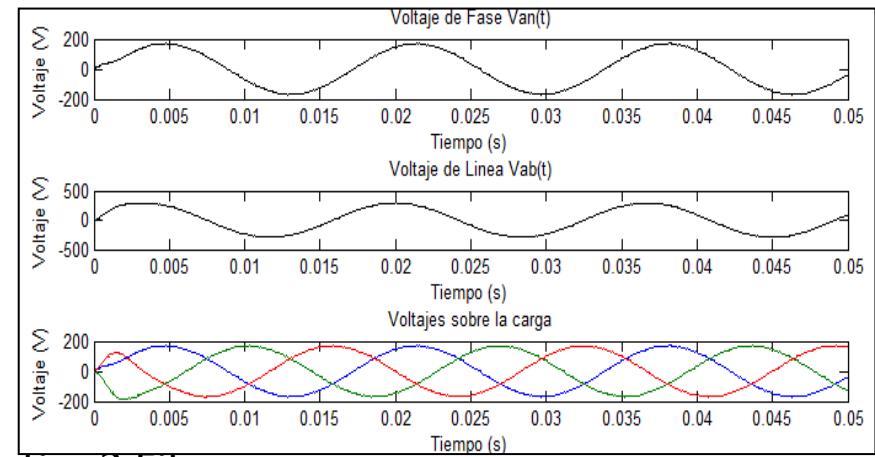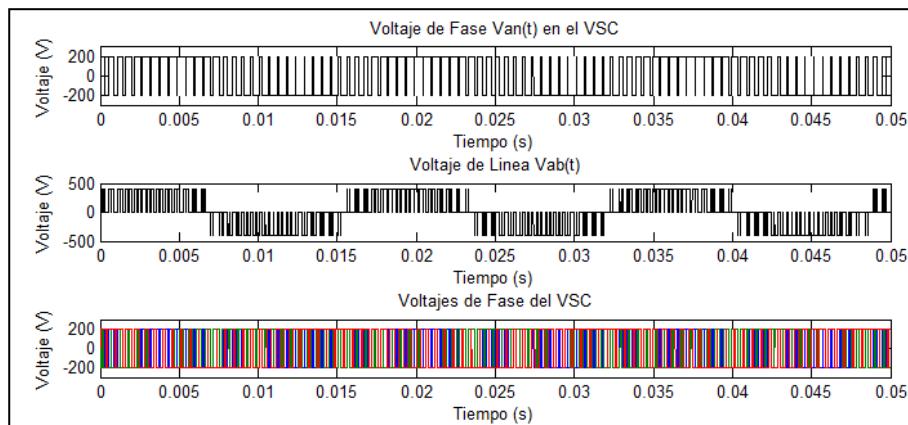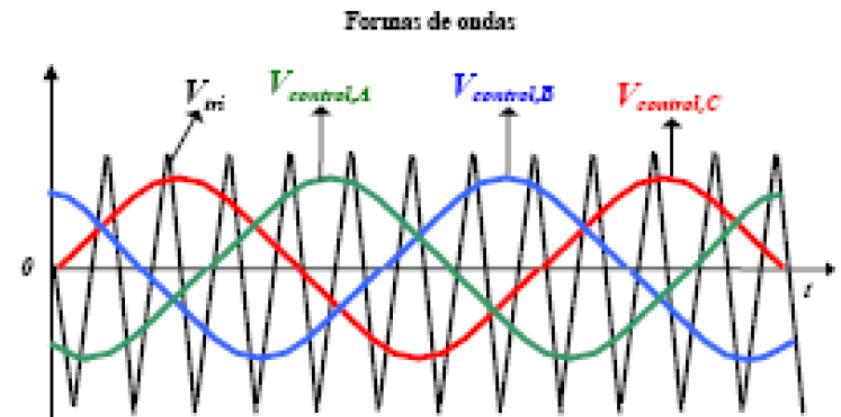

Simulation3 File.

## 2. Power Inverter.

# Filter

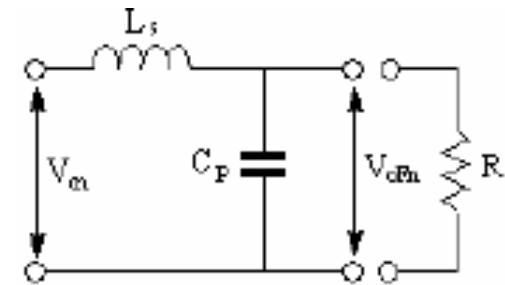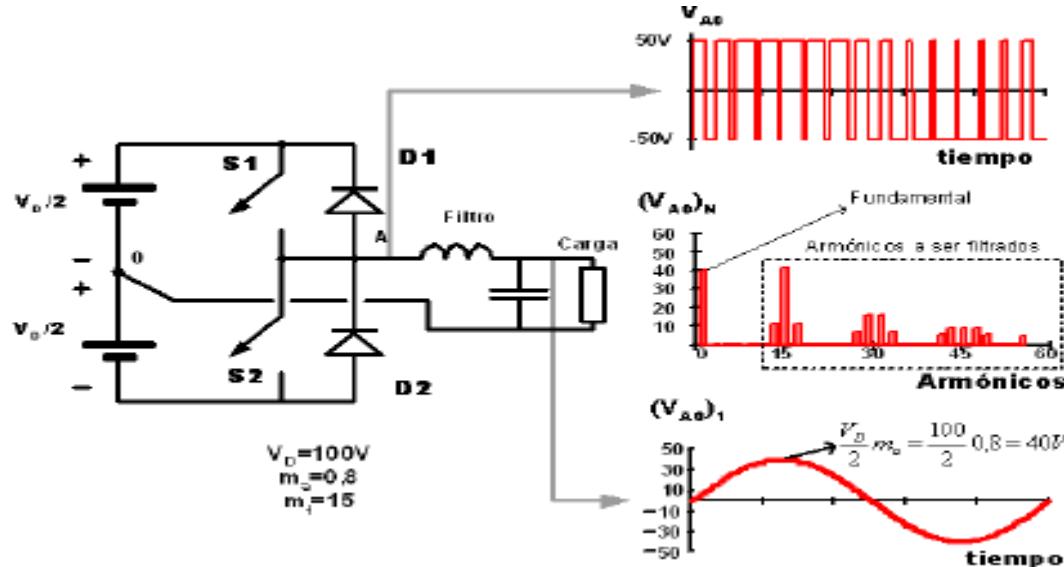

$$T_{mod} \triangleq \frac{1}{f_{res}} \triangleq T_c$$

$$f_{mod} \triangleleft f_{res} \triangleleft f_c$$

$$\frac{V_{out}}{V_{in}} = \frac{L_s + C_p // R}{C_p // R} = \frac{1}{(1 - \omega^2 CL) + \frac{j\omega L}{R}}$$





$$Z_{BASE} = \frac{(V_{base})^2}{S_{base}}$$

$$f_r = \frac{1}{2\pi\sqrt{L_s \times C_p}}$$

$$X = 0.2_{PU} \cdot Z_{BASE}$$



## 2. Power Inverter.

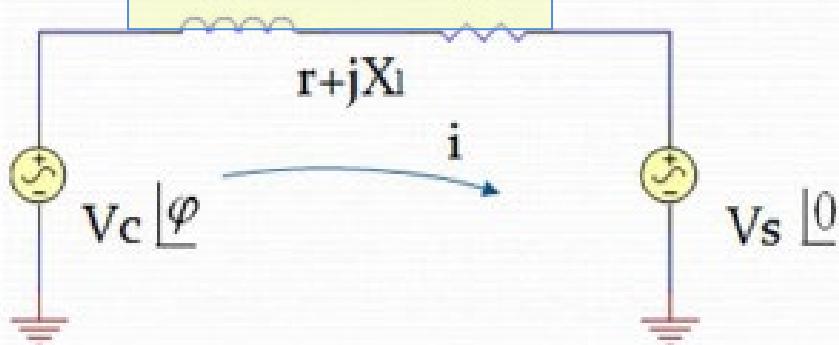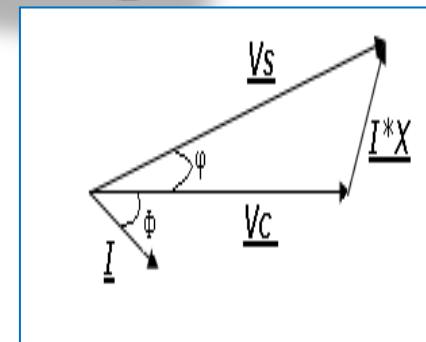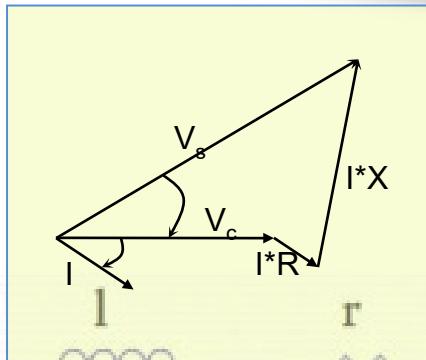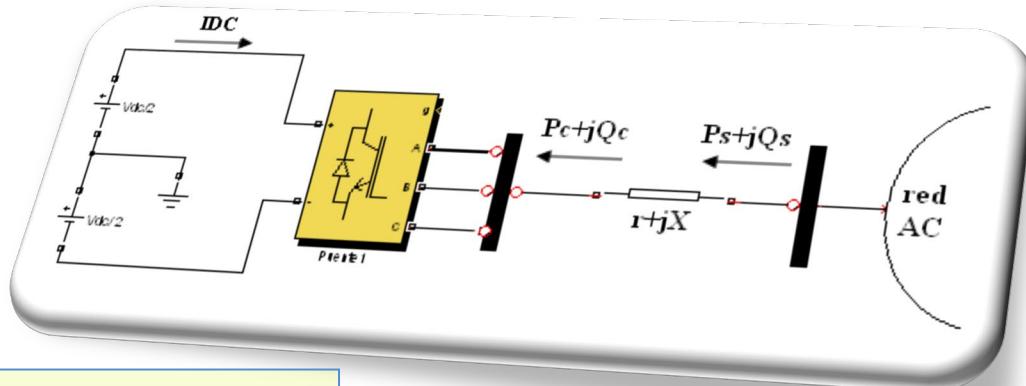


$$P = \frac{V_c \cdot V_s}{X} \sin(\varphi)$$

$$Q = \frac{V_s (-V_s + V_c \cos(\varphi))}{X}$$






## 2. Power Inverter.

---

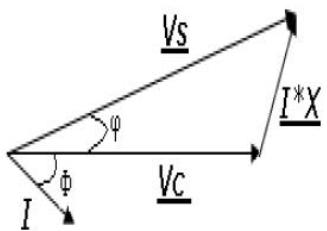

$$P = \frac{V_C \cdot V_S}{X} \sin(\phi)$$
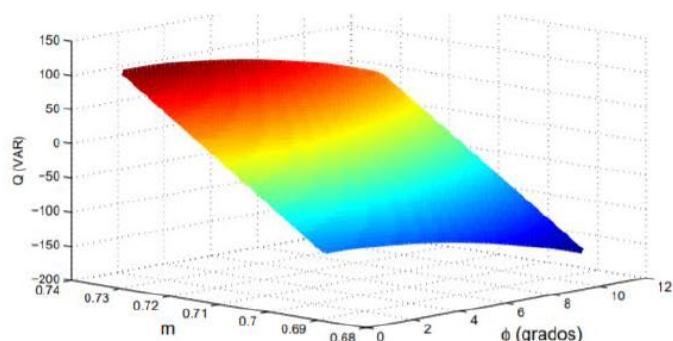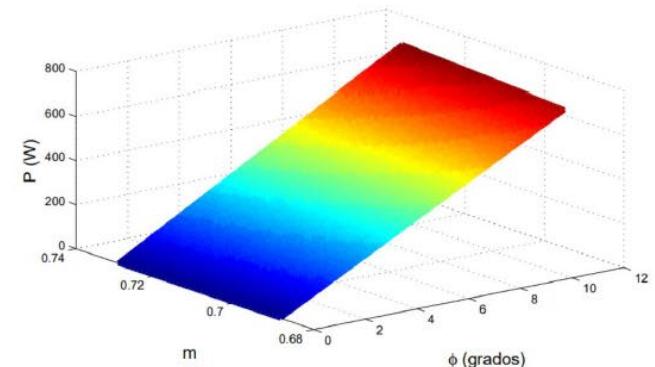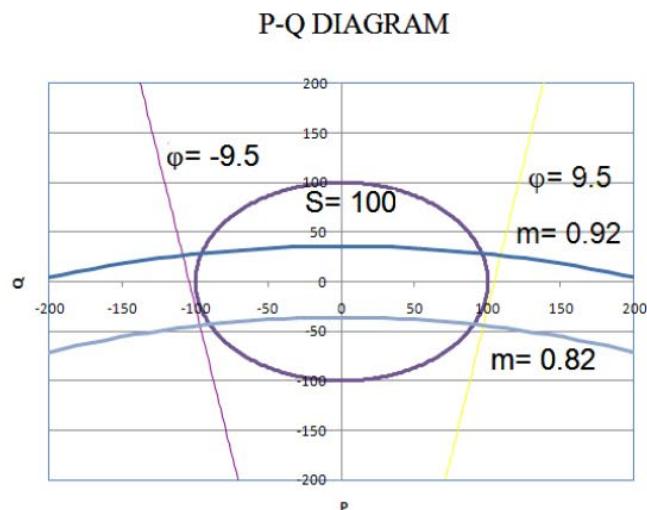
$$Q = \frac{V_S (-V_S + V_C \cos(\phi))}{X}$$



Simulation4 File.

---

Facultad de Ingeniería



## 2. Power Inverter.

---

# Syncronization.



## 2. Power Inverter.

---

Synchronization is an adaptive process in which an automatic system generates an internal oscillator at the frequency and phase of the system it is interconnecting with.

Synchronization handles two main processes:  
Frequency tracking.  
Phase tracking.




## 2. Power Inverter.

---


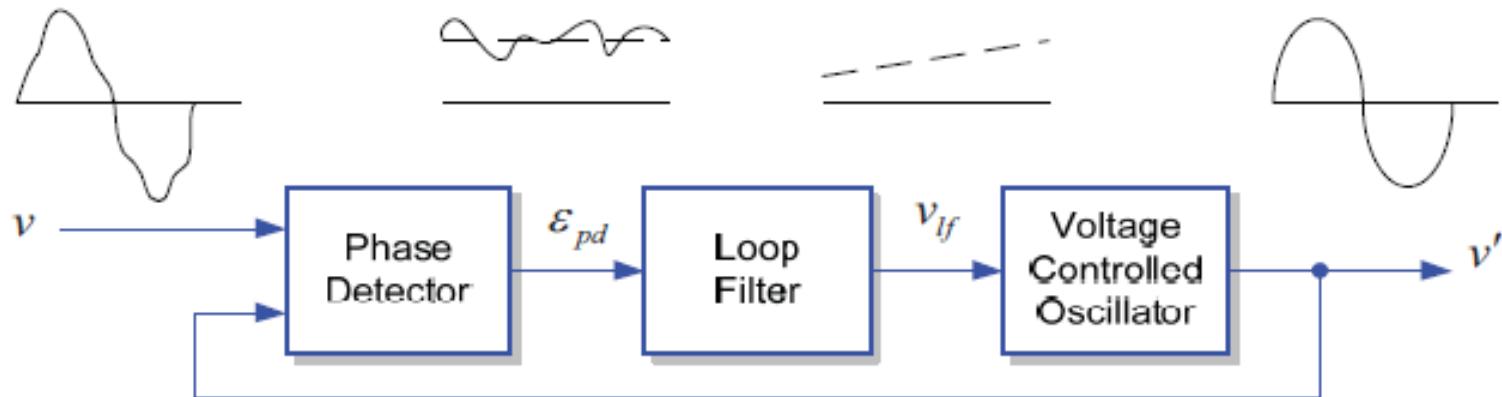
### (Phase Locked Loop) PLL

A PLL is a feedback system that includes a phase detector, a low-pass filter, and a voltage-controlled oscillator (VCO). Its main purpose is to compel the VCO to replicate the frequency and phase of the reference within the loop.



## 2. Power Inverter.

### (Phase Locked Loop) PLL,

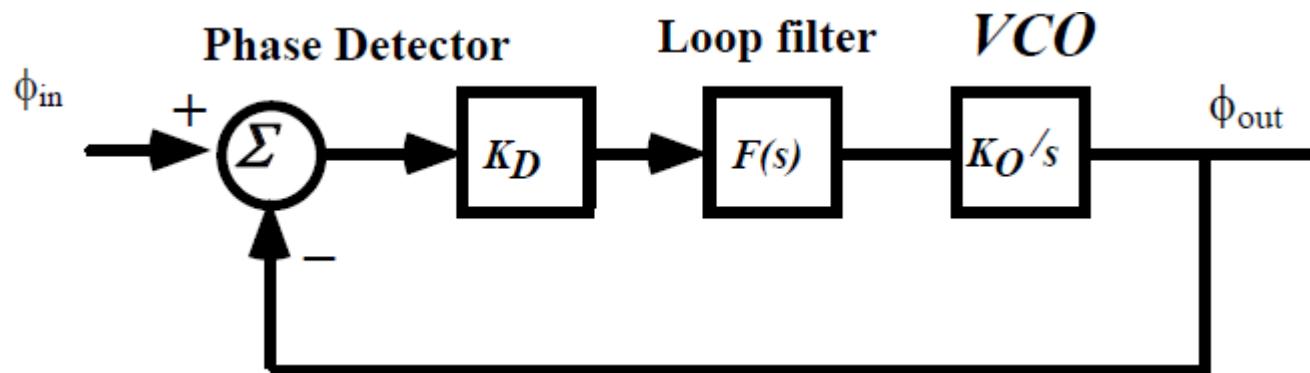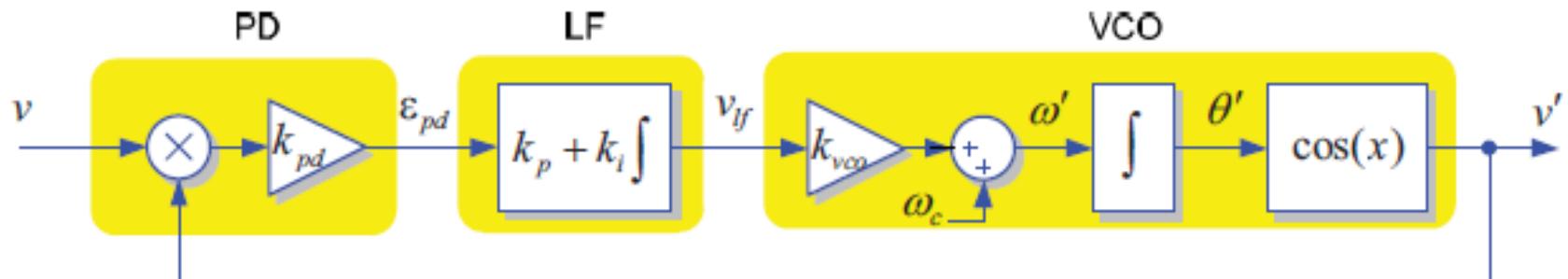


$$H(s) = T(s)/[1 + T(s)]$$

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_D K_O F(s)/s}{1 + K_D K_O F(s)/s}$$



## 2. Power Inverter.
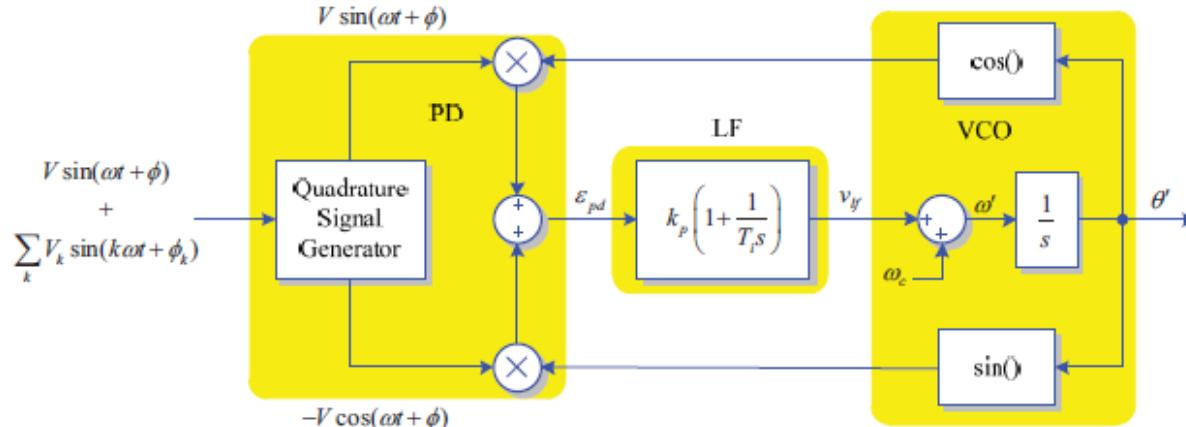
### Phase detector based on Quadrature Signal Generator



- The Quadrature Signal Generator must produce two signals phased 90 degrees apart from a single signal.  $v = V \sin(\theta) = V \sin(\omega t + \phi)$

$$\mathbf{v}_{(\alpha\beta)} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = V \begin{bmatrix} \sin(\omega t + \phi) \\ -\cos(\omega t + \phi) \end{bmatrix} = V \begin{bmatrix} \sin(\theta) \\ -\cos(\theta) \end{bmatrix}$$

- Then:

$$\epsilon_{pd} = V \sin(\omega t + \phi) \cos(\omega' t + \phi') - V \cos(\omega t + \phi) \sin(\omega' t + \phi') = V \sin((\omega - \omega')t + (\phi - \phi')) = V \sin(\theta - \theta')$$


Teodorescu, Liserre, Rodriguez, Grid Connected For Photovoltaic and Wind Power Systems




## 2. Power Inverter.

# Quadrature Signal Generators


- T/4 Delay

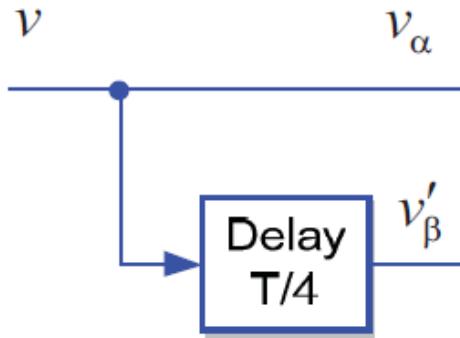

- Tuned Filter

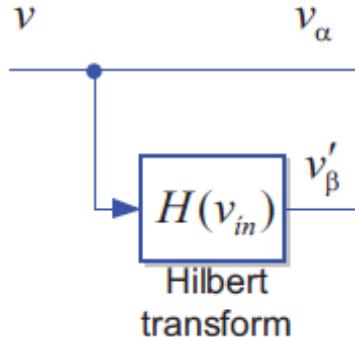
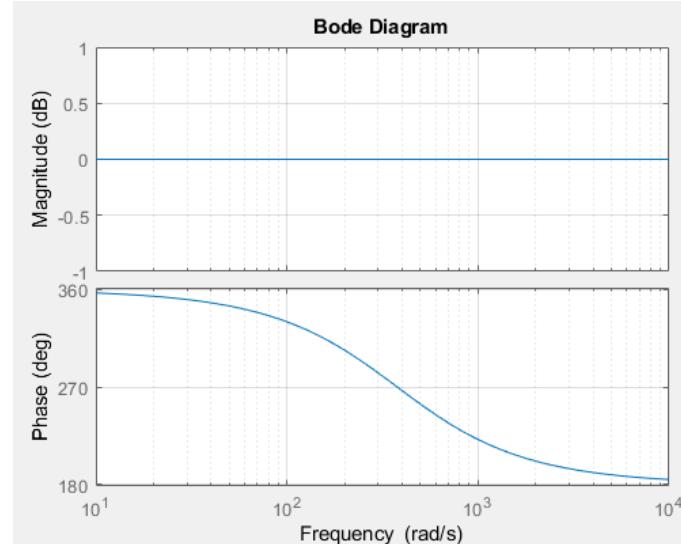
$$H(v_{in}) = \frac{\omega_0 - s}{\omega_0 + s}$$



## 2. Power Inverter.

---



# Park Transformation

- Once we have the phase a quadrature signals:

$$\mathbf{v}_{(\alpha\beta)} = \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = V \begin{bmatrix} \sin(\theta) \\ -\cos(\theta) \end{bmatrix}$$

- The Park Transformation allows transforming time-varying signals into constant signals in a synchronous reference frame (SRF):

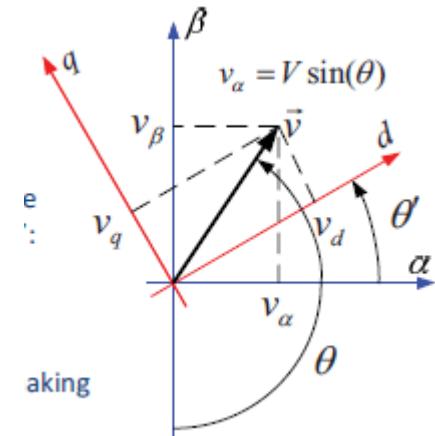
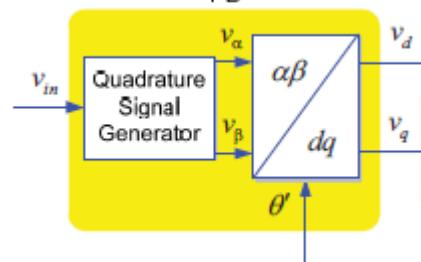
$$\mathbf{v}_{(dq)} = \begin{bmatrix} v_d \\ v_q \end{bmatrix} = \begin{bmatrix} \cos(\theta') & \sin(\theta') \\ -\sin(\theta') & \cos(\theta') \end{bmatrix} \begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = V \begin{bmatrix} \sin(\theta - \theta') \\ -\cos(\theta - \theta') \end{bmatrix}$$



## 2. Power Inverter.


---

# SRF PLL

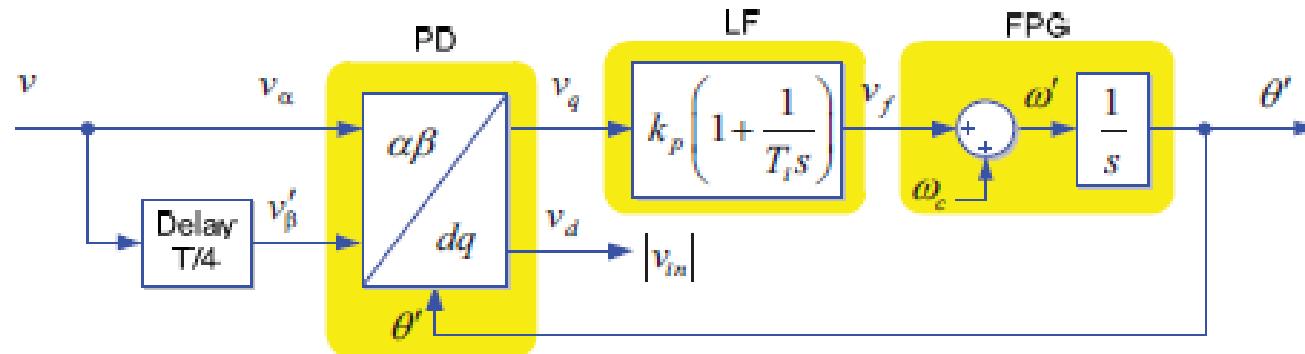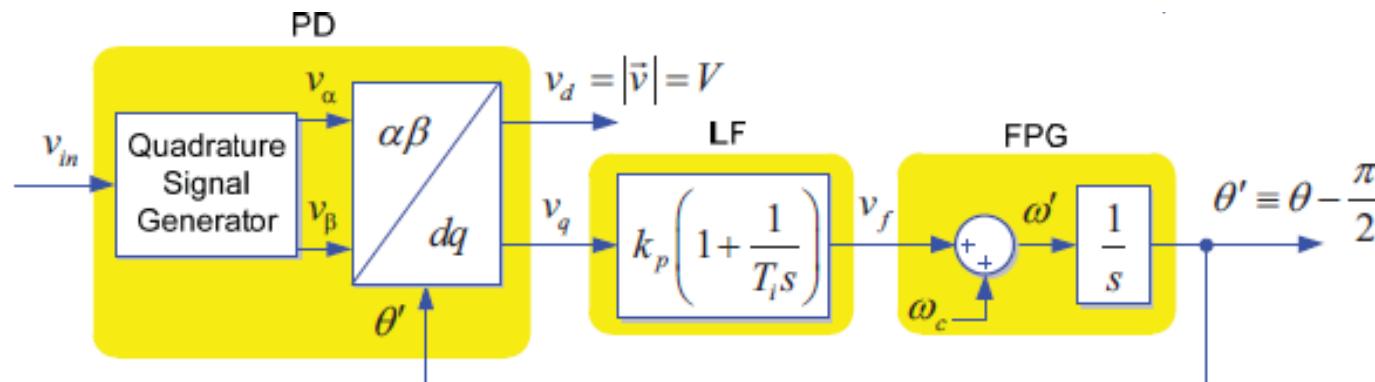

## 2. Power Inverter.

### Excercise

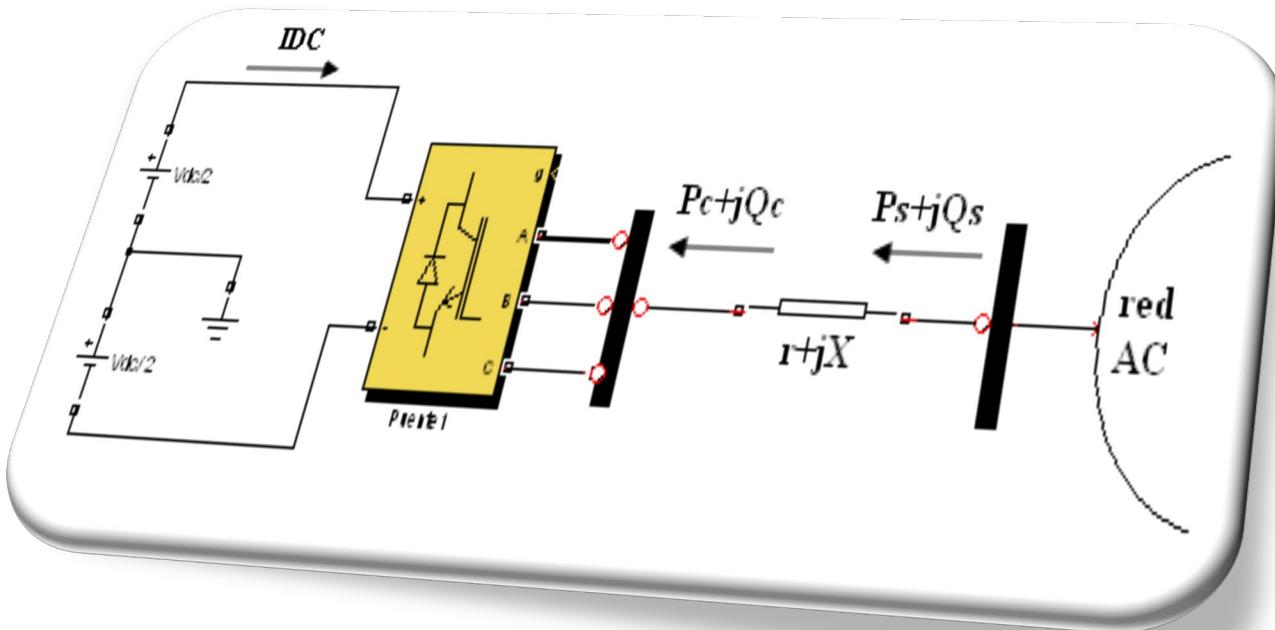

Simulation2, 4, 5 File.

Facultad de Ingeniería



## 2. Power Inverter.

---

# Control and Topological Operation



## 2. Power Converter.

---

### Inner Control Loops


- **Grid Forming Controls:**
  - Voltage Control. (VCM).
  - Frequency.
  - Power Sharing.
  
- **Grid-Following Controls:**
  - Current Control (CCM)
  - Power Export.
  - Power Dispatch.
  - Reactive power support



## 2. Power Converter.

---


### Inner Control Loops

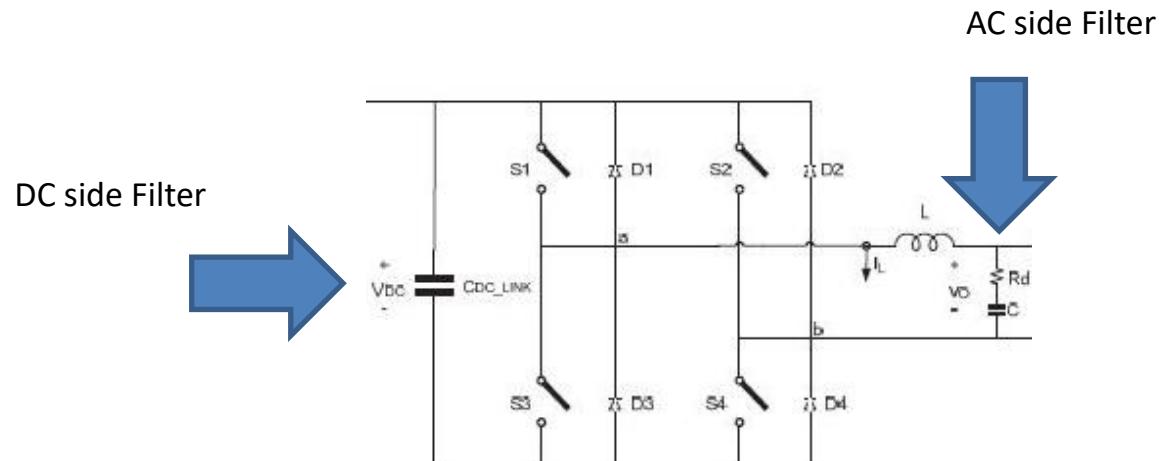

*The Dynamic response depends mainly on the AC and DC Filters.*



## 2. Power Converter.

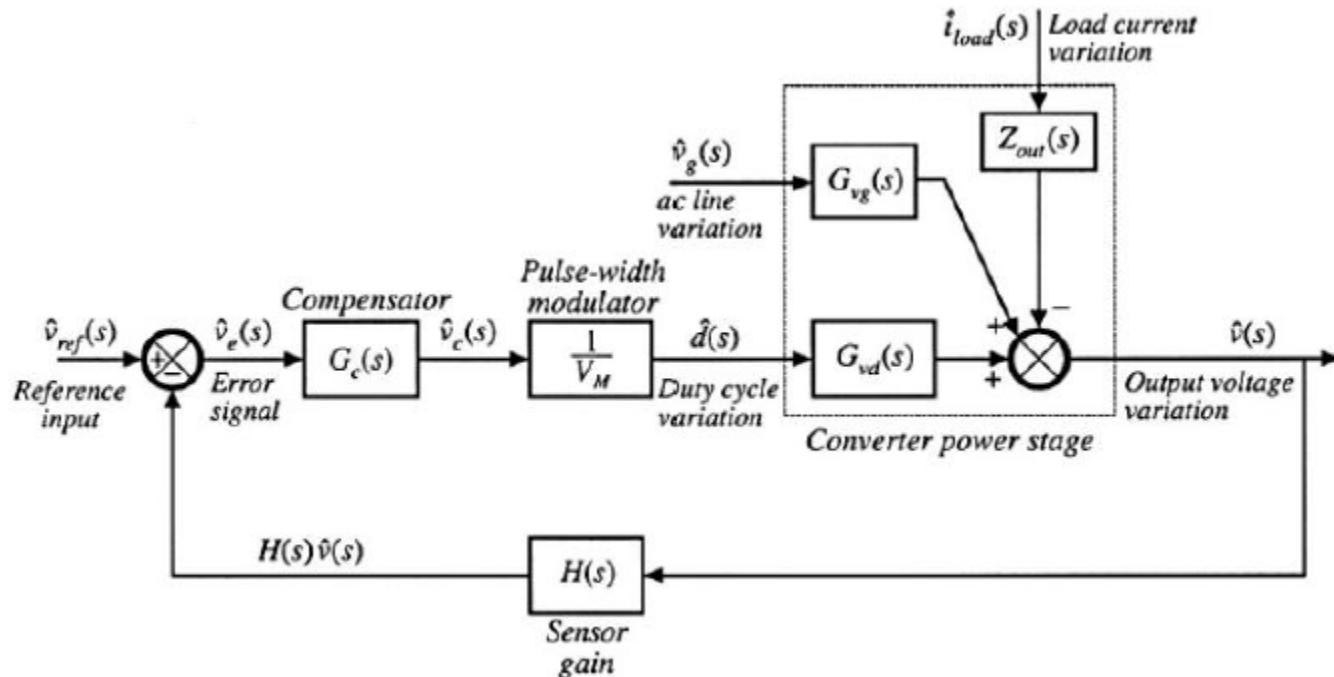


$$\hat{v}(s) = \hat{v}_{ref}(s) \frac{1}{H(s)} \frac{T(s)}{1+T(s)} + \frac{\hat{v}_g(s)}{1+T(s)} - \frac{\hat{i}_{load}}{1+T(s)}$$

*Once the Dynamic model is defined The negative feedback Control loop Will make the system to follows the reference*



## 2. Power Converter.

---

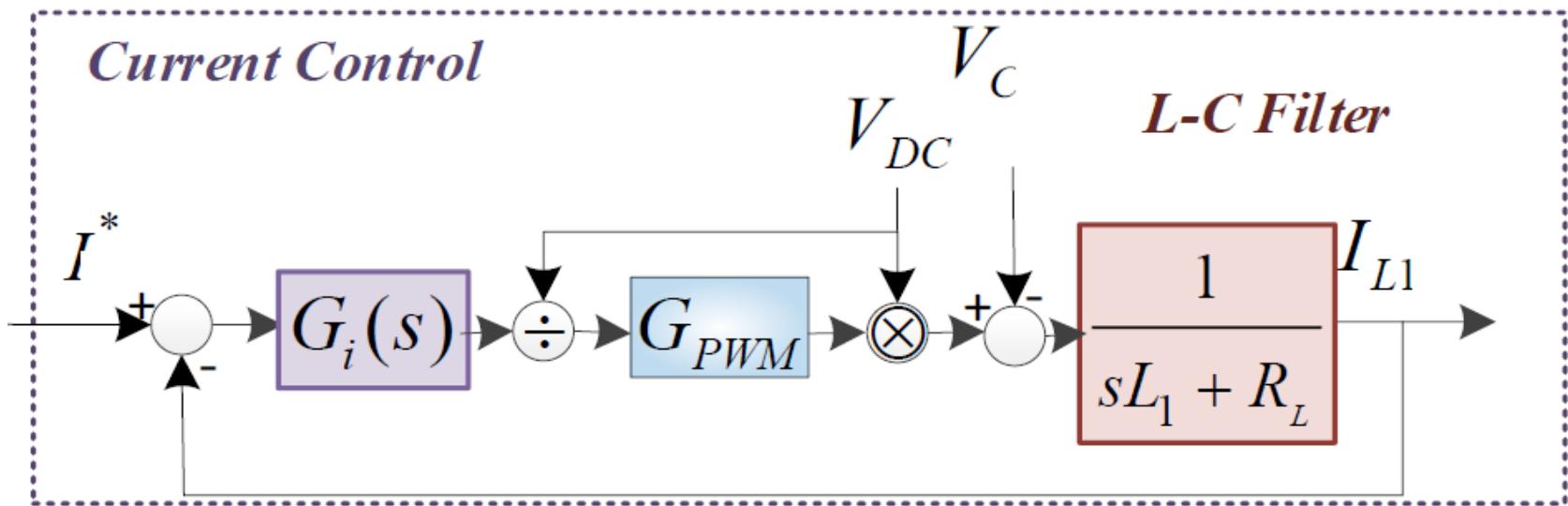

Simulation6 File.

---




Facultad de Ingeniería



## 2. Power Converter.

### Grid-Following

Grid-Following

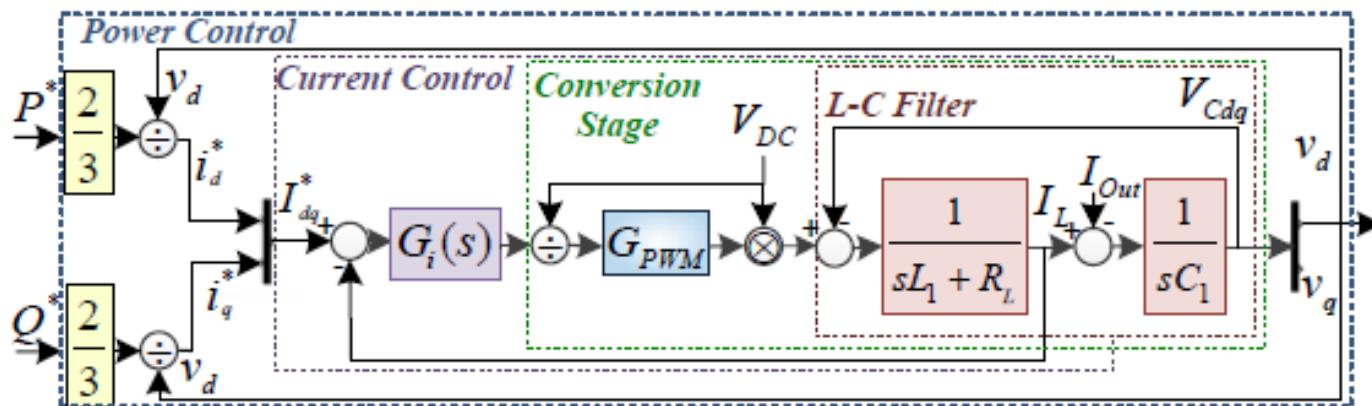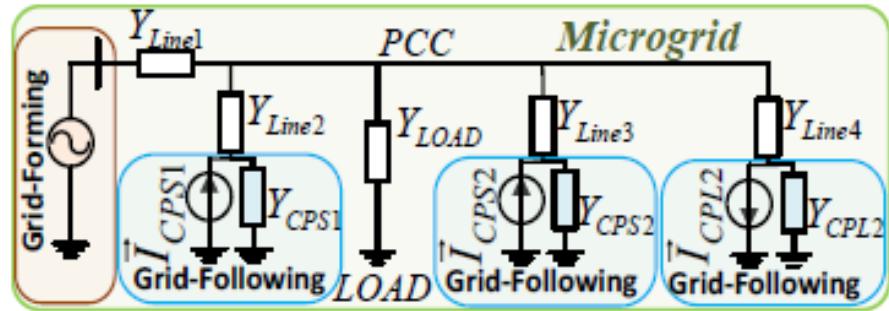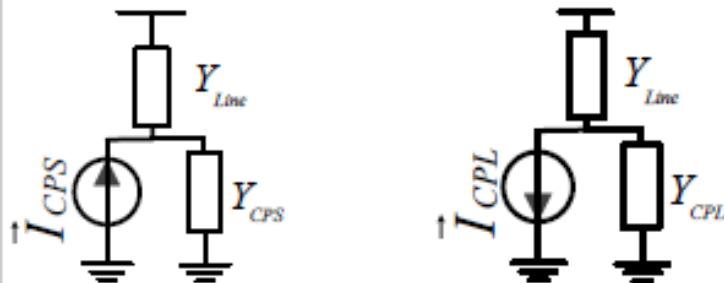

### Current Control Mode (CCM)

Simulation7 File.




Facultad de Ingeniería



## 2. Power Converter.

### Grid-Forming

Grid-Forming

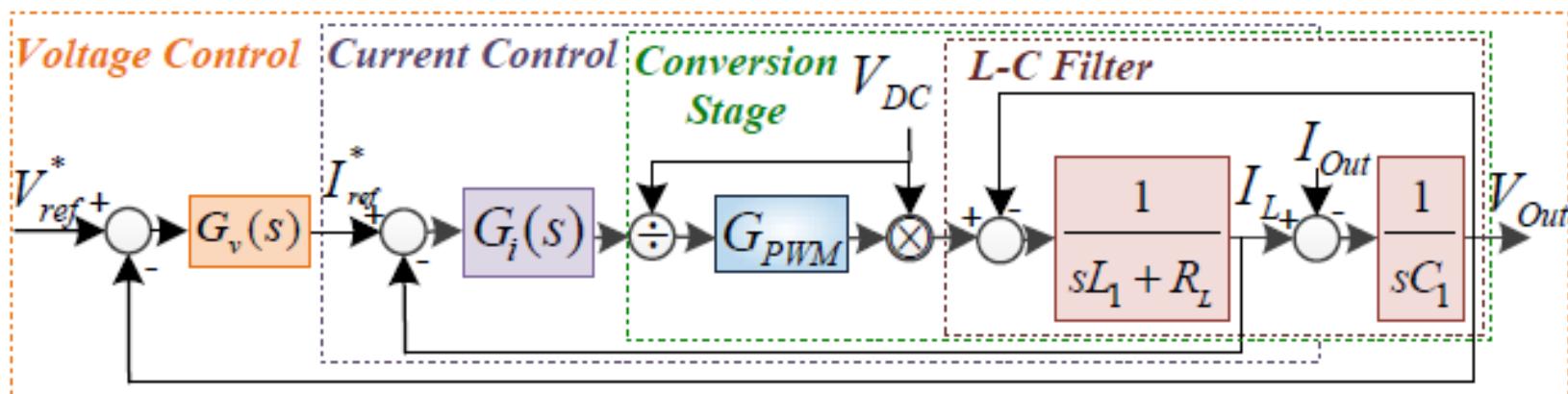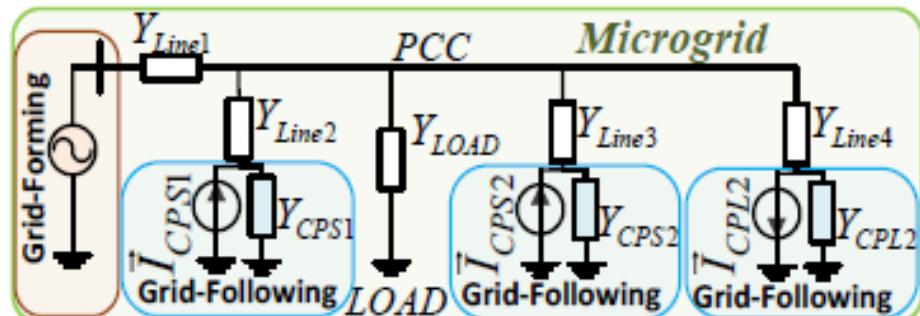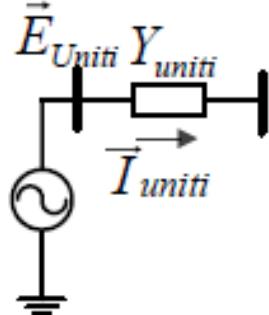

**Voltage Control Mode (VCM)**

Simulation8 File.


Facultad de Ingeniería



## 2. Power Converter.

---

### DC Voltage Control

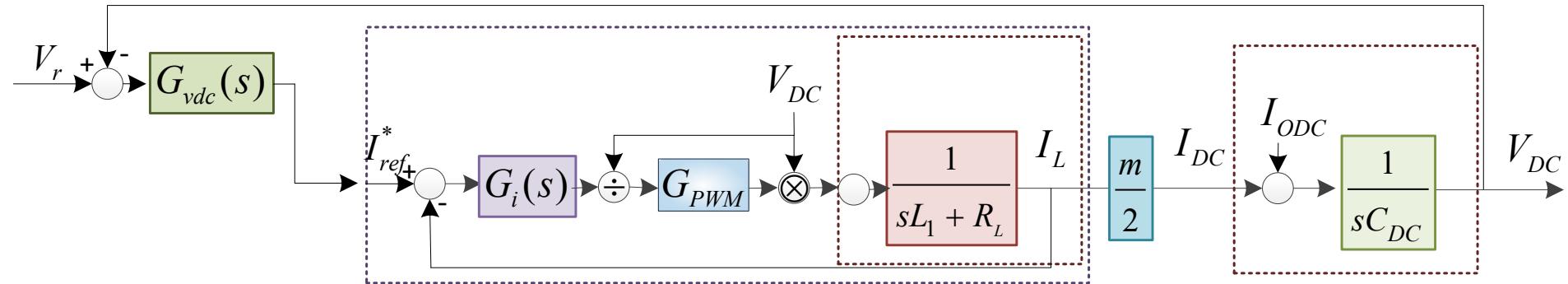

Simulation8 File.

---

Facultad de Ingeniería



# Three Phase Inverter Control


The question is:

Is it necessary to have a control loop per phase in a Three phase system?



## 2. Power Converter.

---

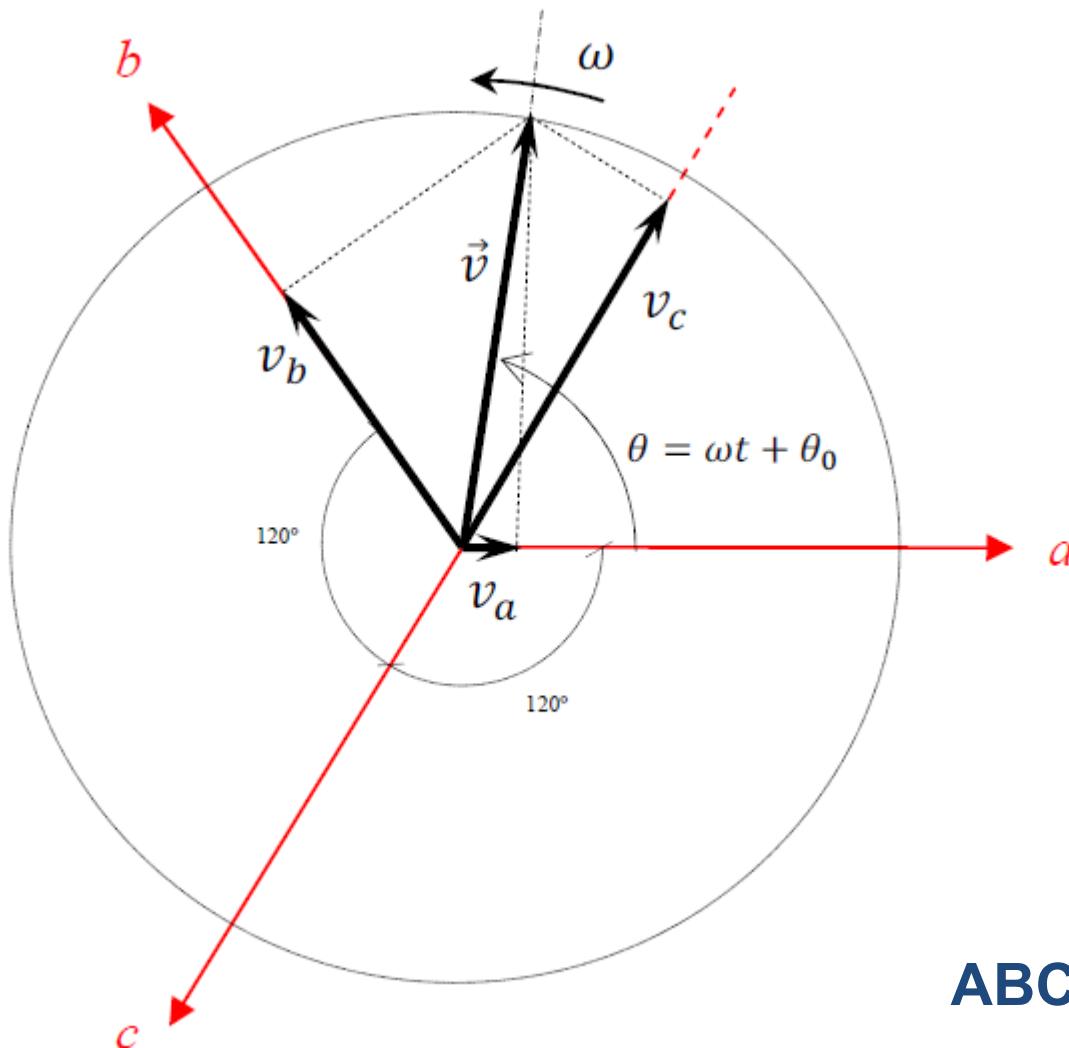


ABC




## 2. Power Converter.

---

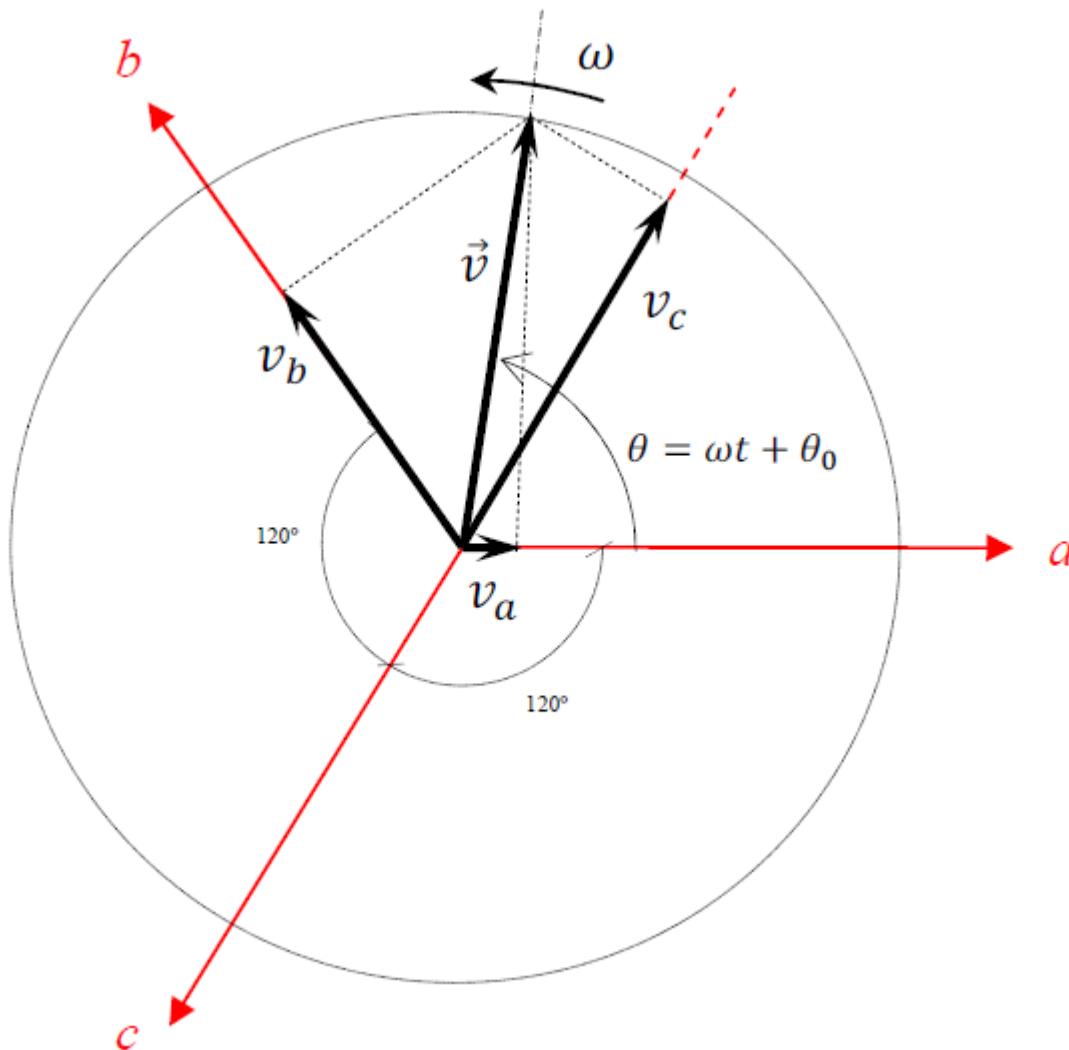

## 2. Power Converter.

### ABC- $\alpha\beta$

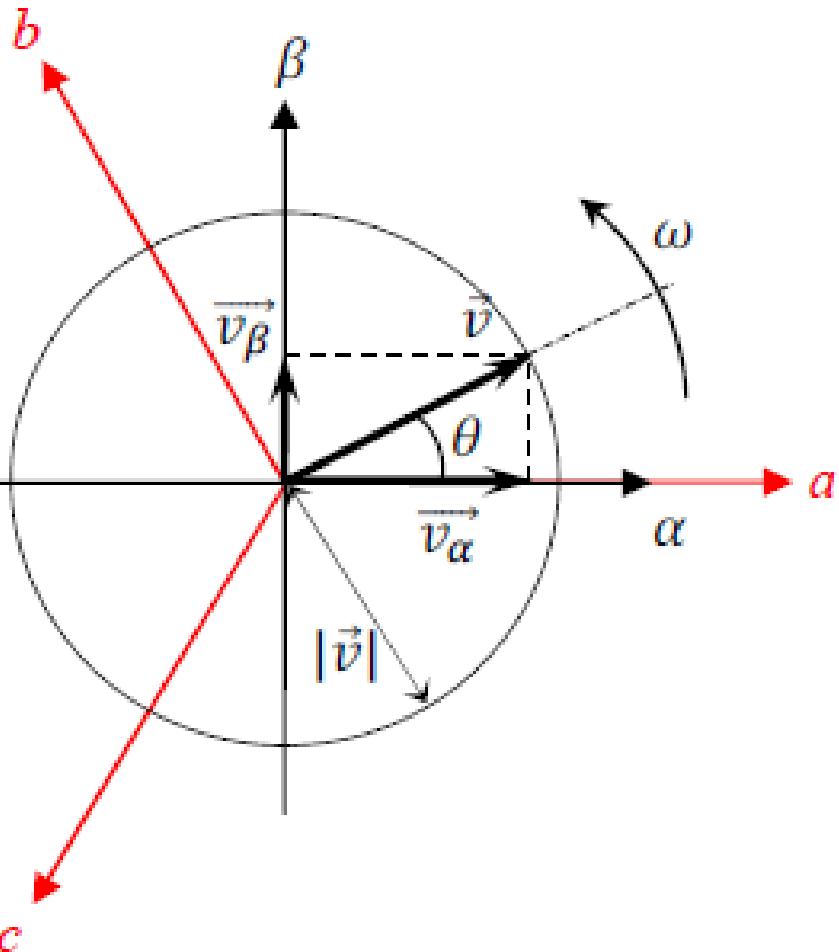

$$v_{abc} = \begin{pmatrix} v_a \\ v_b \\ v_c \end{pmatrix} = v_m \begin{pmatrix} \cos(\theta) \\ \cos(\theta - 2\pi/3) \\ \cos(\theta + 2\pi/3) \end{pmatrix}$$


$$\theta = \omega t + \theta_0$$

$$\begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = [\text{Clarke Matrix}] \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$


$$\begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = \kappa \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$



## 2. Power Converter.

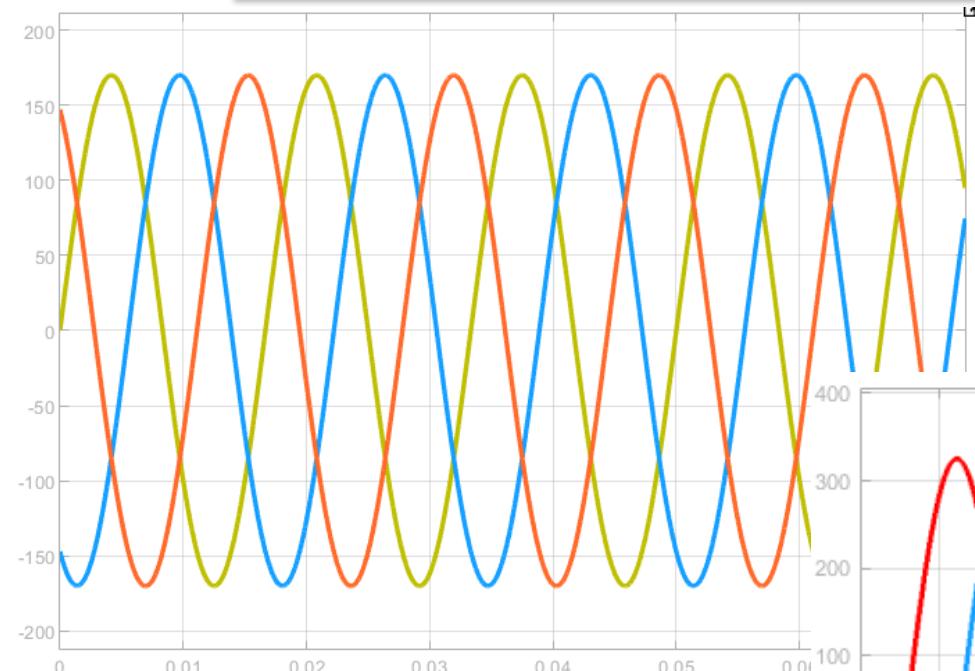
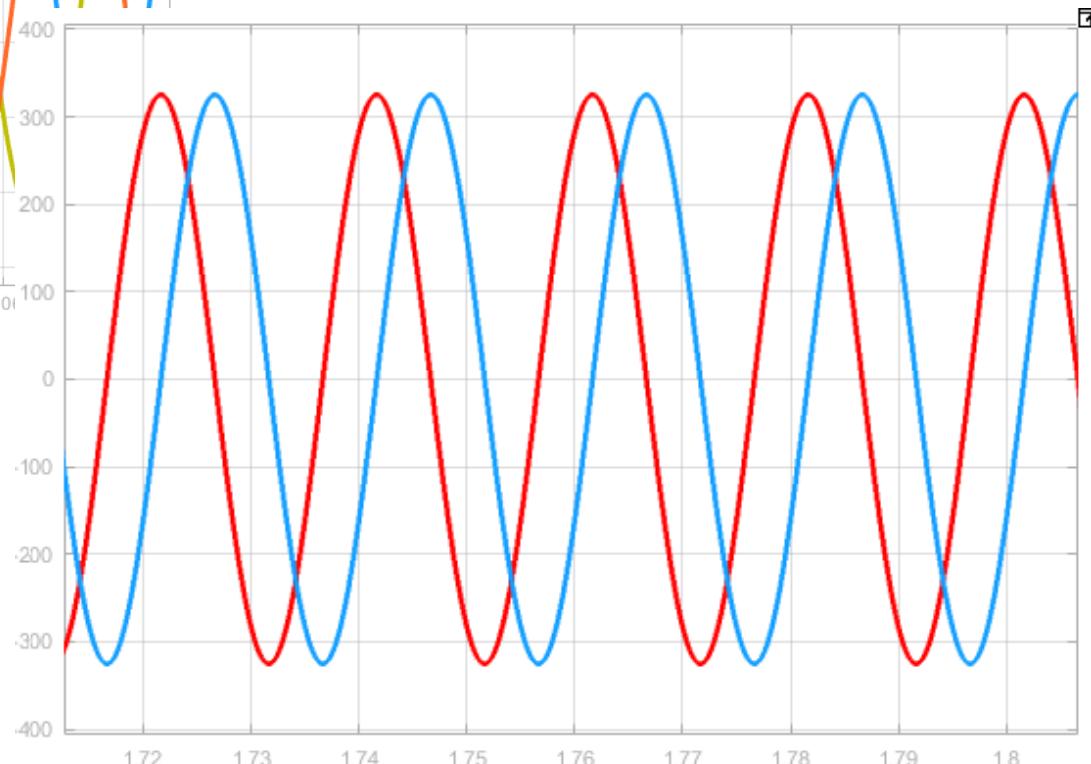
$$\begin{bmatrix} v_\alpha \\ v_\beta \end{bmatrix} = K \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$



ABC- $\alpha\beta$



## 2. Power Converter.

Cte.	Transf.	Inversa	Potencia instantánea trifásica		Escalado
			$p(t)$	$q(t)$	
$\sqrt{2/3}$	T.Clarke	$\mathbf{T}^{-1} = \mathbf{T}^t$	$p = v_\alpha i_\alpha + v_\beta i_\beta$	$q = v_\beta i_\alpha - v_\alpha i_\beta$	$\sqrt{2/3}$
	T.Park	$\mathbf{T}^{-1} = \mathbf{T}^t$	$p = v_d i_d + v_q i_q$	$q = v_q i_d - v_d i_q$	$\sqrt{2/3}$
$2/3$	T.Clarke	$\mathbf{T}^{-1} = \frac{3}{2} \mathbf{T}^t$	$p = \frac{3}{2} (v_\alpha i_\alpha + v_\beta i_\beta)$	$q = \frac{3}{2} (v_\beta i_\alpha - v_\alpha i_\beta)$	$1$
	T.Park	$\mathbf{T}^{-1} = \frac{3}{2} \mathbf{T}^t$	$p = \frac{3}{2} (v_d i_d + v_q i_q)$	$q = \frac{3}{2} (v_q i_d - v_d i_q)$	$1$
$1$	T.Clarke	$\mathbf{T}^{-1} = \frac{2}{3} \mathbf{T}^t$	$p = \frac{2}{3} (v_\alpha i_\alpha + v_\beta i_\beta)$	$q = \frac{2}{3} (v_\beta i_\alpha - v_\alpha i_\beta)$	$3/2$
	T.Park	$\mathbf{T}^{-1} = \frac{2}{3} \mathbf{T}^t$	$p = \frac{2}{3} (v_d i_d + v_q i_q)$	$q = \frac{2}{3} (v_q i_d - v_d i_q)$	$3/2$

Same Power Value in  $\alpha\beta$  and abc


Same voltage and current value in  $\alpha\beta$  and abc



## 2. Power Converter.


---

PLL

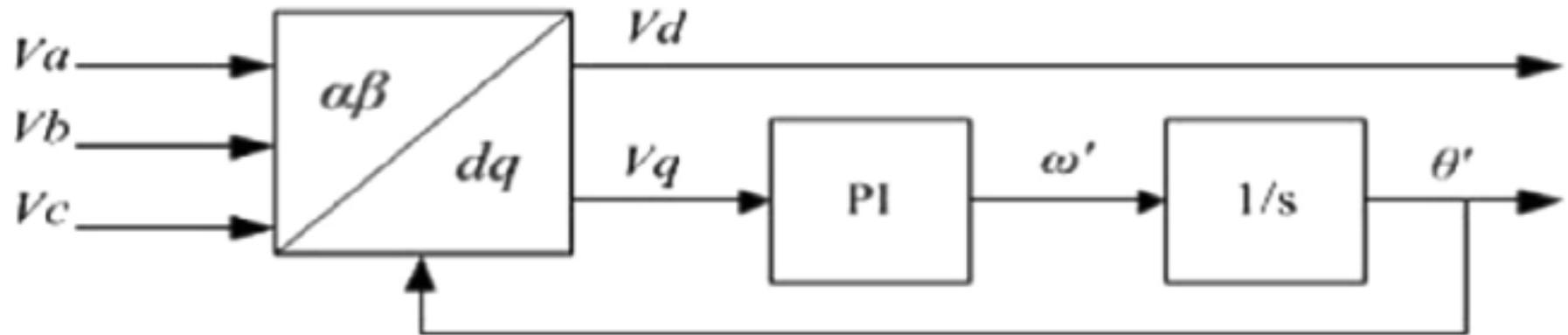

## 2. Power Converter.

### $\alpha\beta$ Control

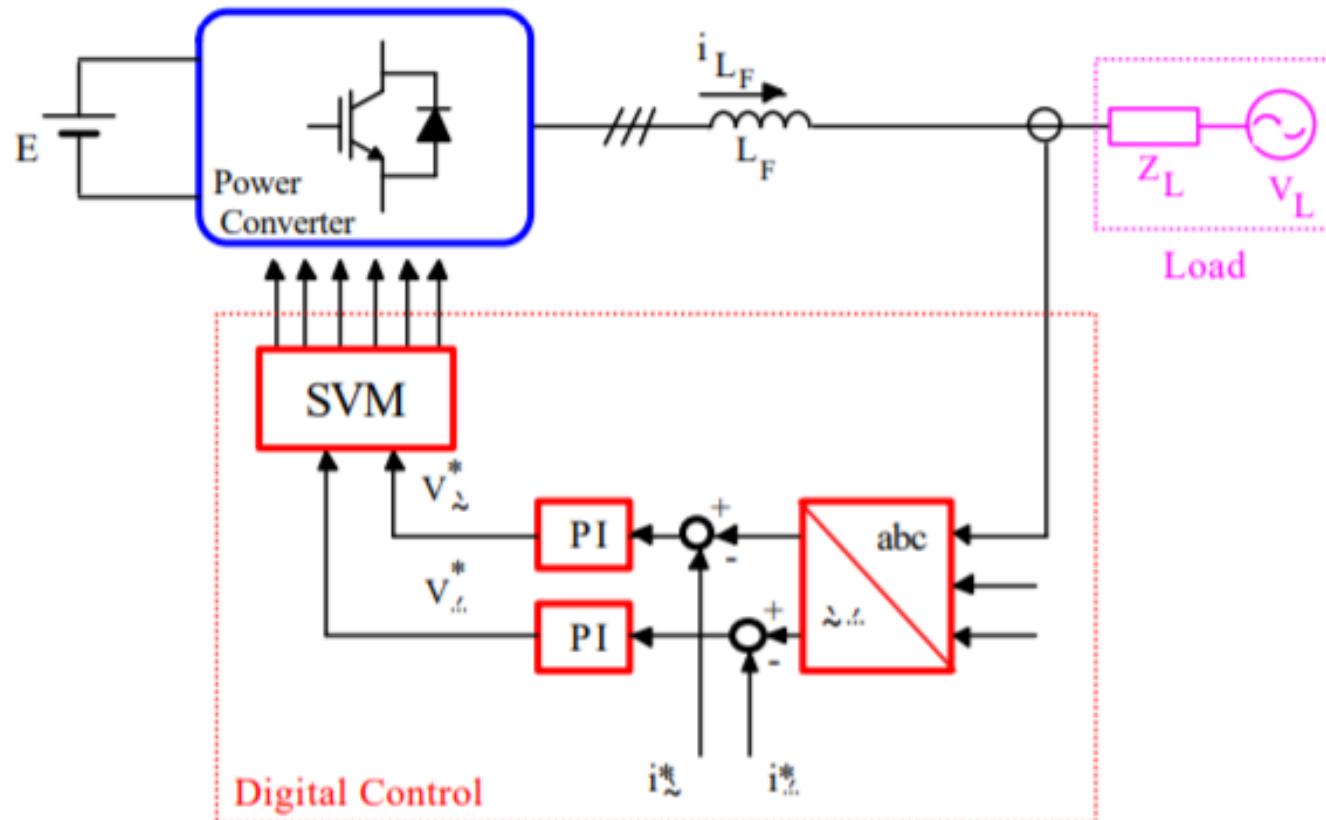


Simulation8 File.

Facultad de Ingeniería



## 2. Power Converter.

$\alpha\beta$ -DQ

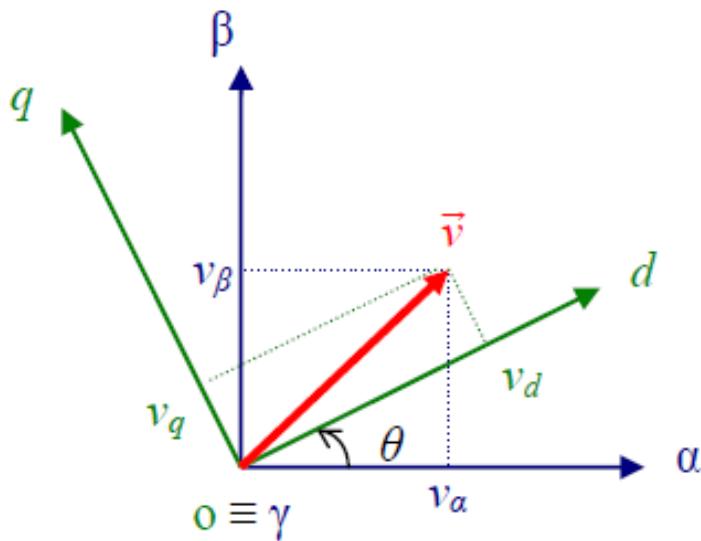

$$\begin{bmatrix} d \\ q \end{bmatrix} = \begin{bmatrix} \cos \theta & \sin \theta \\ -\sin \theta & \cos \theta \end{bmatrix} \times \begin{bmatrix} \alpha \\ \beta \end{bmatrix}$$


$$\begin{bmatrix} d \\ q \end{bmatrix} = [\text{Park Matrix}] \times \begin{bmatrix} \alpha \\ \beta \end{bmatrix}$$

$$\begin{bmatrix} d \\ q \end{bmatrix} = [\text{Park Matrix}] \times [\text{Clarke Matrix}] \times \begin{bmatrix} A \\ B \\ C \end{bmatrix}$$



## 2. Power Converter.

ABC-DQ

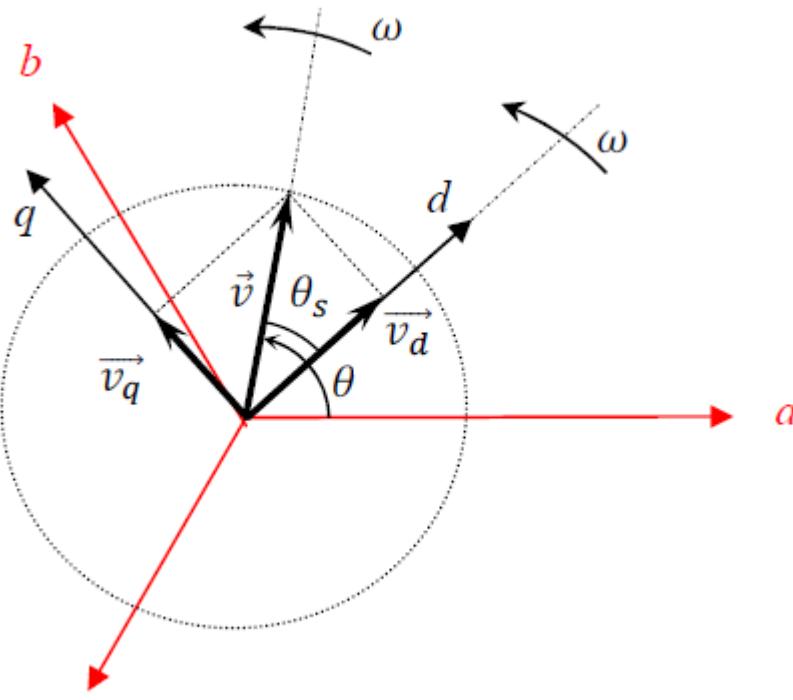


$$\begin{bmatrix} f_d \\ f_q \end{bmatrix} = \frac{2}{3} \begin{bmatrix} \cos(\alpha t) & \cos(\alpha t - \frac{2}{3}\pi) & \cos(\alpha t + \frac{2}{3}\pi) \\ -\sin(\alpha t) & -\sin(\alpha t - \frac{2}{3}\pi) & -\sin(\alpha t + \frac{2}{3}\pi) \end{bmatrix} \cdot \begin{bmatrix} f_a \\ f_b \\ f_c \end{bmatrix}$$



## 2. Power Converter.

### DQ-Control

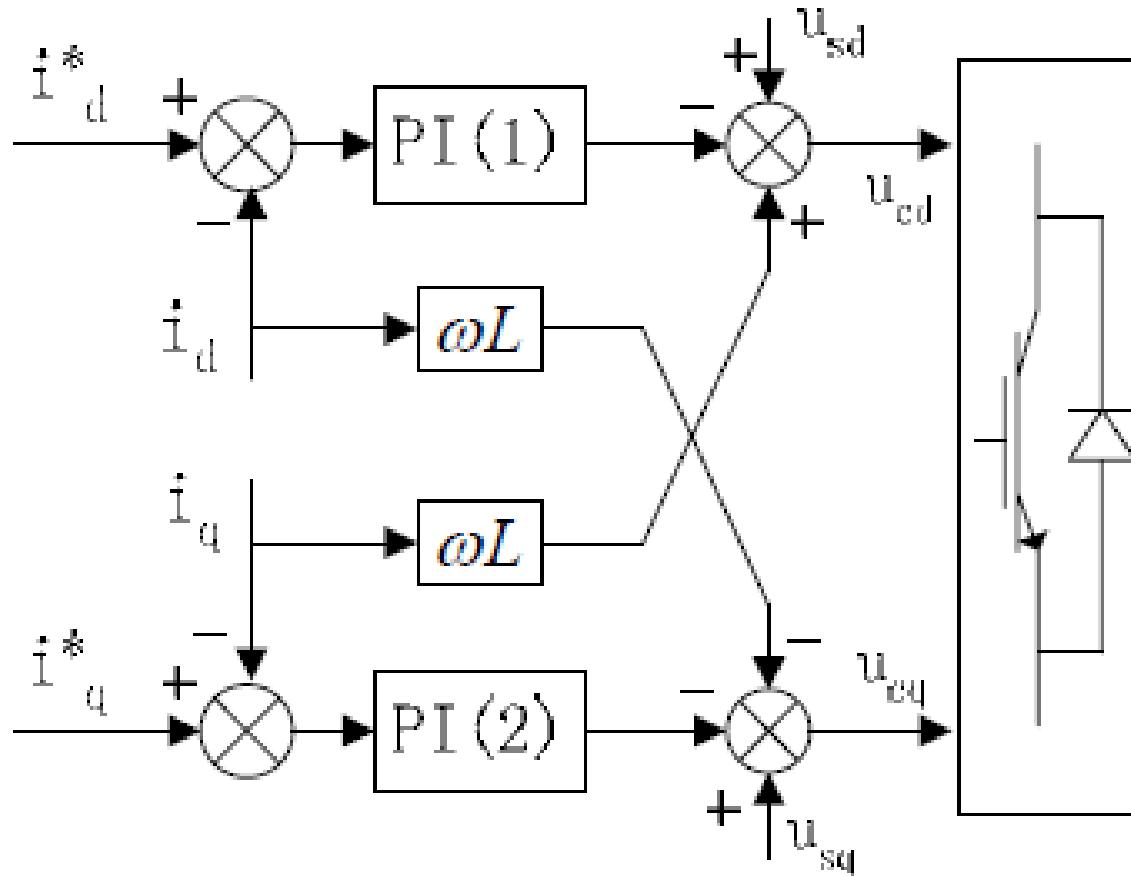

In a Three phase system we need three signals for the SPWM. What to do?

$$\delta_{an}(t) = \frac{1}{2} + \frac{1}{2}m * \sin(\omega t + \varphi)$$

$$\delta_{bn}(t) = \frac{1}{2} + \frac{1}{2}m * \sin\left(\omega t - \frac{2\pi}{3} + \varphi\right)$$

$$\delta_{cn}(t) = \frac{1}{2} + \frac{1}{2}m * \sin(\omega t + 2\pi/3 + \varphi)$$


*Inverse transformation*



## 2. Power Converter.

---
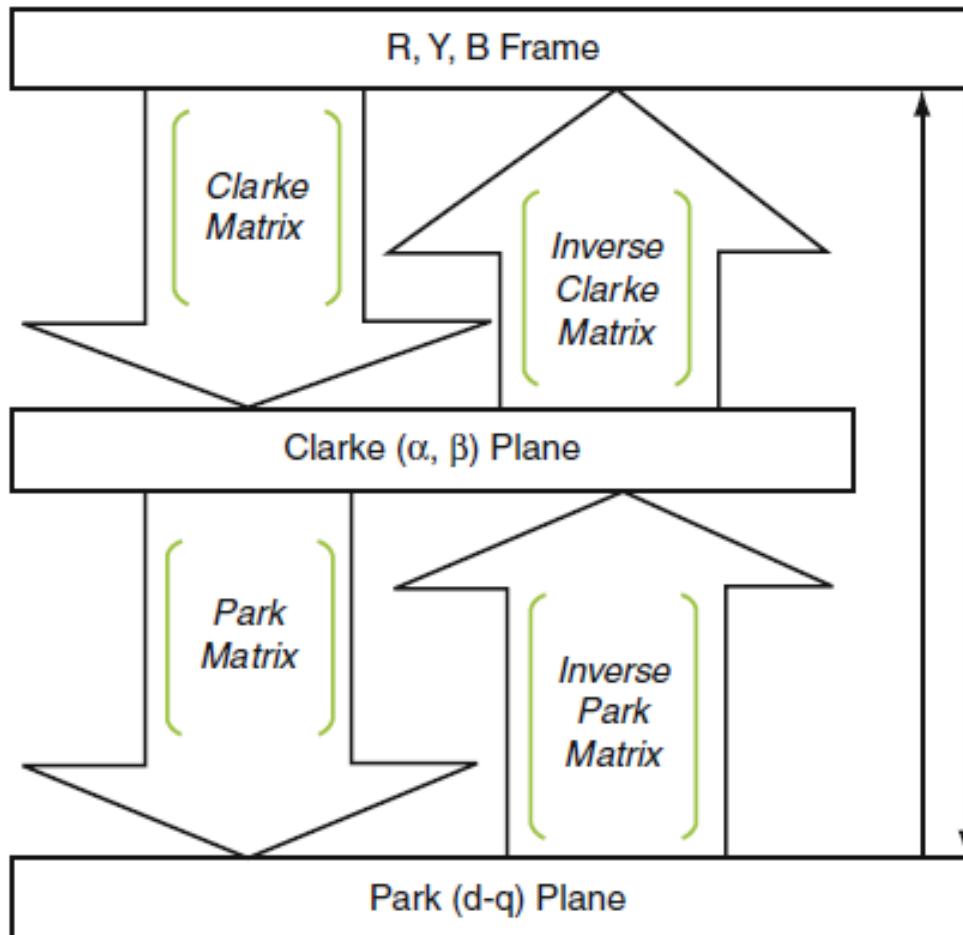
### ABC- $\alpha\beta$ -DQ- $\alpha\beta$ -ABC



## 2. Power Converter.

---

### Inverse Transformation

$$[T] \cdot [T]^T = \sqrt{\frac{2}{3}} \cdot T \cdot \sqrt{\frac{2}{3}} \cdot T^T = \frac{2}{3} \cdot T \cdot T^T = [I]_{3 \times 3} \quad \Rightarrow \quad [T]^T = [T]^{-1}$$

$$\begin{bmatrix} \alpha \\ \beta \end{bmatrix} = [\text{Inverse Park Matrix}] \times \begin{bmatrix} d \\ q \end{bmatrix}$$

$$\begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} \cos \theta & -\sin \theta \\ \sin \theta & \cos \theta \end{bmatrix} \times \begin{bmatrix} d \\ q \end{bmatrix}$$

$$i_{abc}(t) = T^{-1} i_{\alpha\beta\gamma}(t) = \begin{bmatrix} 1 & 0 & 1 \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} & 1 \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} & 1 \end{bmatrix} \begin{bmatrix} i_\alpha(t) \\ i_\beta(t) \\ i_\gamma(t) \end{bmatrix}.$$




## 2. Power Converter.

Cte.	Transf.	Inversa	Potencia instantánea trifásica		Escalado
			$p(t)$	$q(t)$	
$\sqrt{2/3}$	T.Clarke	$\mathbf{T}^{-1} = \mathbf{T}^t$	$p = v_\alpha i_\alpha + v_\beta i_\beta$	$q = v_\beta i_\alpha - v_\alpha i_\beta$	$\sqrt{2/3}$
	T.Park	$\mathbf{T}^{-1} = \mathbf{T}^t$	$p = v_d i_d + v_q i_q$	$q = v_q i_d - v_d i_q$	$\sqrt{2/3}$
$2/3$	T.Clarke	$\mathbf{T}^{-1} = \frac{3}{2} \mathbf{T}^t$	$p = \frac{3}{2} (v_\alpha i_\alpha + v_\beta i_\beta)$	$q = \frac{3}{2} (v_\beta i_\alpha - v_\alpha i_\beta)$	1
	T.Park	$\mathbf{T}^{-1} = \frac{3}{2} \mathbf{T}^t$	$p = \frac{3}{2} (v_d i_d + v_q i_q)$	$q = \frac{3}{2} (v_q i_d - v_d i_q)$	1
1	T.Clarke	$\mathbf{T}^{-1} = \frac{2}{3} \mathbf{T}^t$	$p = \frac{2}{3} (v_\alpha i_\alpha + v_\beta i_\beta)$	$q = \frac{2}{3} (v_\beta i_\alpha - v_\alpha i_\beta)$	$3/2$
	T.Park	$\mathbf{T}^{-1} = \frac{2}{3} \mathbf{T}^t$	$p = \frac{2}{3} (v_d i_d + v_q i_q)$	$q = \frac{2}{3} (v_q i_d - v_d i_q)$	$3/2$



## 2. Power Converter.

---

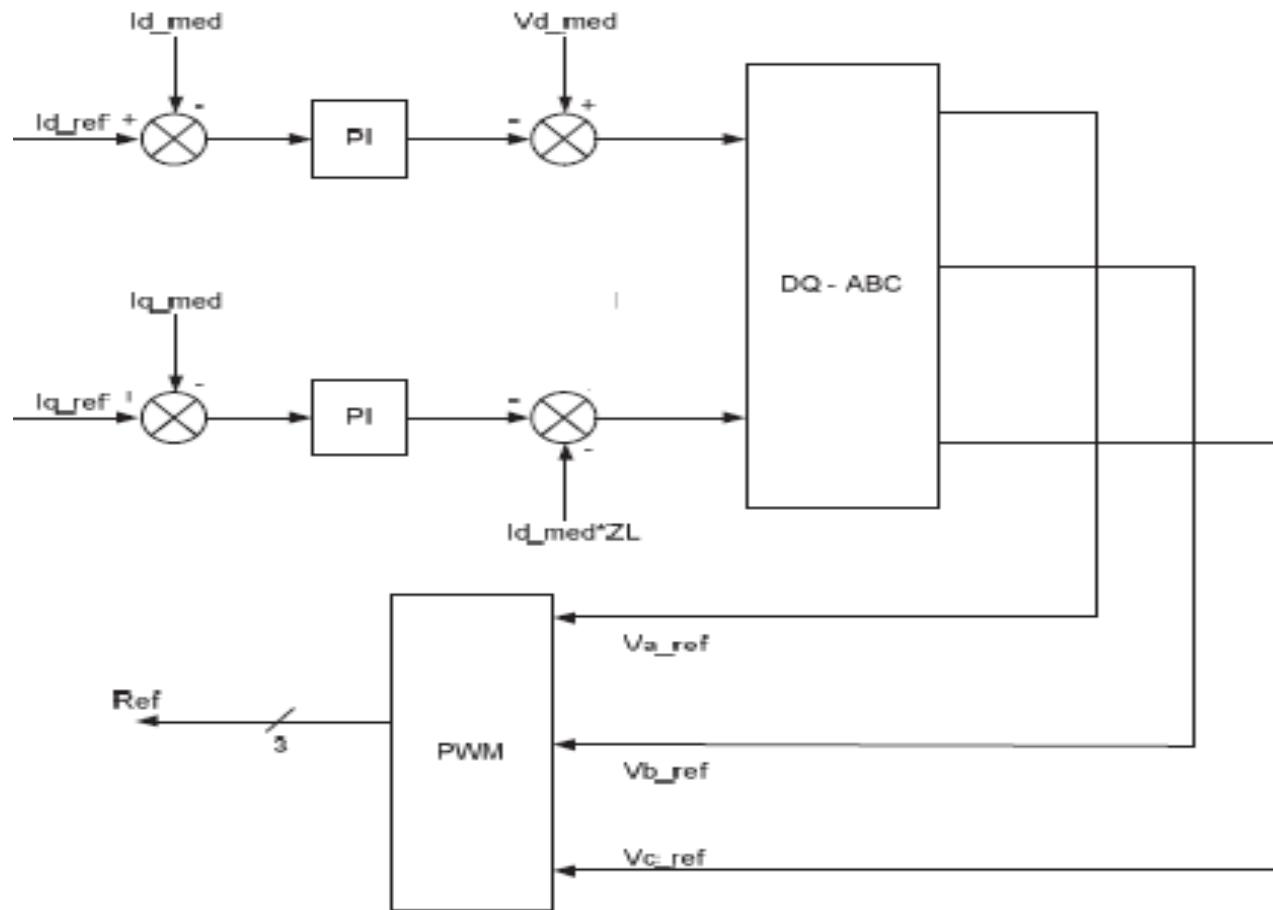

---

Simulation 10, 11, 12 File.

Facultad de Ingeniería



## 2. Power Converter.



---

# Interaction of Power Converters





## 2. Power Converter.

---

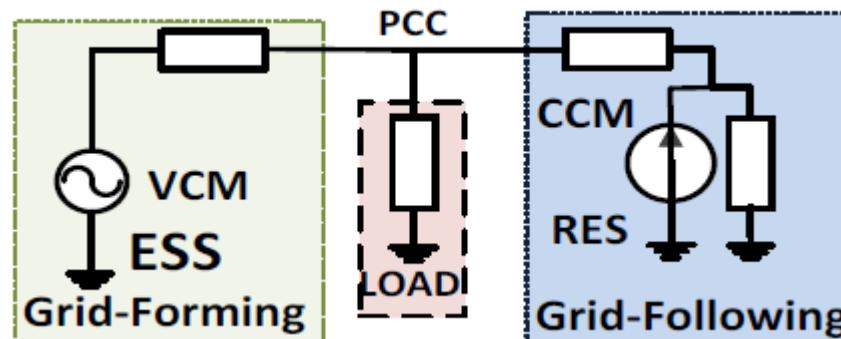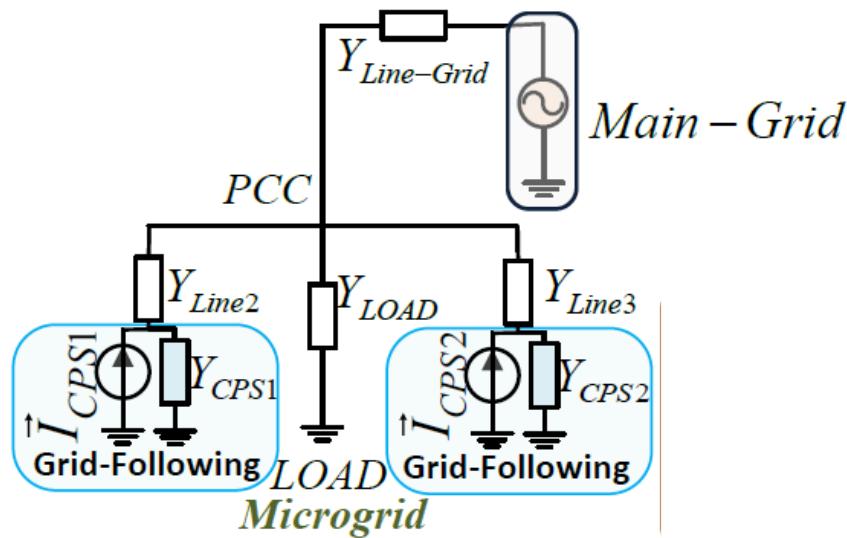

## 2. Power Converter.

---

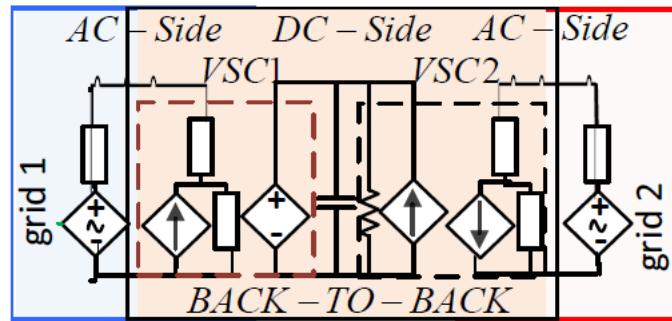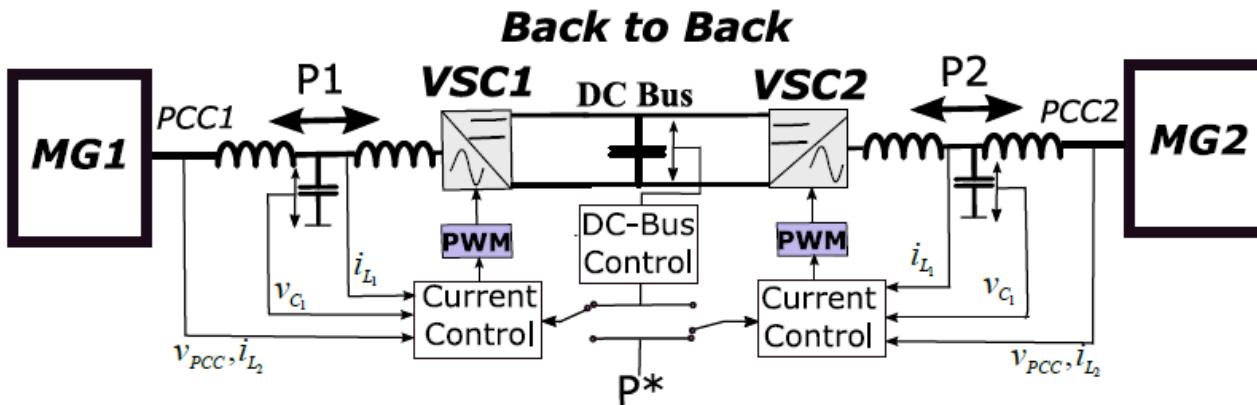

## 2. Power Converter.

---

